 


Lab05 Lecture Exercise

1. The following is a single-bit partial comparator similar to what you modeled and synthesized in week 4's lab. According to what you learned today, this comparator is a *component*.

```

ENTITY comp_1 IS
PORT ( A, B : IN      STD_LOGIC;
        Y : OUT   STD_LOGIC
        );
END comp_1;
    
```




```

ARCHITECTURE Algebraic OF comp_1 IS      -- ARCHITECTURE tells us about the inside of circuit.
    SIGNAL T, U, W: STD_LOGIC;              -- Intermediate signals
BEGIN
    Y <= (U NAND W);
    W <= (B NAND T);
    U <= (A NAND T);
    T <= (A NAND B);
END Algebraic;
    
```

Based on what you see above:

- What is the *component's* name?
- What are the *formals* of the component?

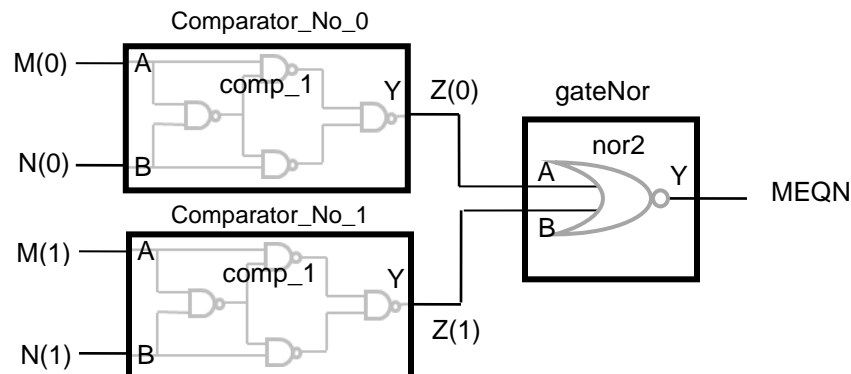Using the above component, you are going to *structurally* model a 2-bit partial comparator in VHDL. The structural model is *graphically* shown below. As you see, there are two instances of the above component in this 2-bit partial comparator. Additionally, a second component called nor2 is used with only one instance:



- What is the name of the first *instance* of comp_1 (the one on the top)?
- Write the *actuals* of the second instance of comp_1:

- A 4-bit partial comparator is **structurally** modeled here. Make all the necessary changes to convert it to a 2-bit comparator:

```
ENTITY comp_4h IS
PORT (M, N : IN      STD_LOGIC_VECTOR (3 DOWNT0 0);
      MEQN : OUT     STD_LOGIC  -- Active-high output
      );
END comp_4h;
```

ARCHITECTURE Structure OF comp_4h IS

```
    SIGNAL Z: STD_LOGIC_VECTOR (3 DOWNT0 0);  -- Intermediate signals
```

```
    COMPONENT comp_1
    PORT (A, B : IN      STD_LOGIC;
          Y : OUT     STD_LOGIC
          );
    END COMPONENT;
```

```
    COMPONENT nor4
    PORT (A, B, C, D: IN      STD_LOGIC;
          Y : OUT     STD_LOGIC
          );
    END COMPONENT;
```

BEGIN

```
    First_Comparator: comp_1
    PORT MAP (M(0), N(0), Z(0));
```

```
    Second_Comparator: comp_1
    PORT MAP (M(1), N(1), Z(1));
```

```
    Third_Comparator: comp_1
    PORT MAP (M(2), N(2), Z(2));
```

```
    Fourth_Comparator: comp_1
    PORT MAP (M(3), N(3), Z(3));
```

```
    -- NOR gate is added structurally (not algebraically)
    -- NOR gate needs its own file (entity and architecture) not shown here.
    -- You need to compile ALL the files when doing simulation or synthesis.
```


```
    gateNor: nor4
    PORT MAP (Z(3), Z(2), Z(1), Z(0), MEQN);
```

END Structure;

 2. The entity of a component called `dcd` is shown here:

```
ENTITY dcd IS
  PORT (  s1, s0      : IN      STD_LOGIC;
          OUT00,
          OUT01,
          OUT11      : OUT     STD_LOGIC
        );
END dcd;
```

This component asserts output `OUT00`, `OUT01` or `OUT11` when binary values 00, 01 or 11, respectively, are applied to inputs `s1s0`. Scott, who has not taken Digital Systems I yet (but digital design is his hobby), wants to use this `dcd` to control a light, a door and an alarm as shown in the following test bench. **Note** that the actuals associated with formals `OUT00`, `OUT01` and `OUT11` are `TurnLightOn`, `OpenDoor` and `SoundAlarm`, respectively:



Therefore,

If `SW1:0` are set to 00, then the light should turn on.

If `SW1:0` are set to 01, then the door should open.

If `SW1:0` are set to 11, then the alarm should sound.

Here is how Scott has instantiated `dcd`:

```
Controller: dcd PORT MAP (SW(1), SW(0), OpenDoor, SoundAlarm TurnLightOn);
```

Unfortunately, he realizes a weird operation when he tests his controller:

When he wants to open the door, the alarm sounds instead!

When he tries to sound the alarm, the light turns on instead!

When he wants to turn the light on, the door opens instead!

Help Scott figure out what is wrong with his design, and then correct it.