

Digital Systems I

Lab06-07 Slides based on **Chapter 5 - Part II**

Behavioral Modeling of Digital Circuits


Conditional Signal Assignments
and

Selected Signal Assignments

N. Tabrizi

Kettering University


Row	D1	D0	S	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

 


$$M = S \cdot D1 + S' \cdot D0$$

M <= (NOT S AND D0) OR (S AND D1);

Simple Signal Assignment ☺

 

Simple Signal Assignment ☹

 


```
M <= D1 WHEN S = '1' ELSE D0;
```

Conditional Signal Assignment


In this specific example,
Order is unimportant

```
M <=  A WHEN S = "00" ELSE  
      B WHEN S = "01" ELSE  
      C WHEN S = "10" ELSE  
      D;
```

-- Use " " for vectors

 

Conditional Signal Assignment

 

```


M <=  A WHEN S = "00" ELSE
      B WHEN S = "01" ELSE
      D;

```

-- Use " " for vectors

Conditional Signal Assignment

Binary Decoders

 

EN_N	S	L
0	00	0001
0	01	0010
0	10	0100
0	11	1000
1	xx	0000

Binary Decoders

Now

order is important!

```
L <= "0000" WHEN EN_N = '1' ELSE  
     "0001" WHEN S = "00" ELSE  
     "0010" WHEN S = "01" ELSE  
     "0100" WHEN S = "10" ELSE  
     "1000" ;
```

EN_N	S	L
0	00	0001
0	01	0010
0	10	0100
0	11	1000
1	xx	0000

Lab06 Lecture Exercise

Look at the following VHDL code:

```
L <=  "1111" WHEN      EN   = '0'   ELSE
      "1110" WHEN      S   =  "00"   ELSE
      "1101" WHEN      S   =  "01"   ELSE
      "1011" WHEN      S   =  "10"   ELSE
      "0111" ;
```

Which frequently used digital circuit is described by this code?

Are the outputs active-high or active-low?

active-high

active-low

Is the Enable input (EN) active-high or active-low?

active-high

active-low

We get this if the first two lines are swapped:

```
L <=  "1110"      WHEN S =  "00"   ELSE
      "1111"      WHEN EN =  '0'    ELSE
      "1101"      WHEN S =  "01"   ELSE
      "1011"      WHEN S =  "10"   ELSE
      "0111" ;
```

Give a counterexample to show that the above two codes are not equivalent: (fill in the blanks)

EN = S = L in 1st code = L in 2nd code =

Fill in the blank:

In this example, the order of WHEN ELSE lines is ...

Important

Unimportant

Write an input value that generates the same output for both codes:

EN =

S =


If the last 2 WHEN ELSE lines are swapped, will the meaning of the code change?

Yes

No

Priority Encoders


7: Highest

 

R0	R1	R2	R3	R4	R5	R6	R7	N2	N1	N0	No Req
x	x	x	x	x	x	x	1	1	1	1	0
x	x	x	x	x	x	1	0	1	1	0	0
x	x	x	x	x	1	0	0	1	0	1	0
x	x	x	x	1	0	0	0	1	0	0	0
x	x	x	1	0	0	0	0	0	1	1	0
x	x	1	0	0	0	0	0	0	1	0	0
x	1	0	0	0	0	0	0	0	0	1	0
1	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	x	x	x	1

Priority Encoders

7: Highest

 

```

N <=  "111"  WHEN R(7) = '1'  ELSE -- Highest
      "110"  WHEN R(6) = '1'  ELSE
      "101"  WHEN R(5) = '1'  ELSE
      "100"  WHEN R(4) = '1'  ELSE
      "011"  WHEN R(3) = '1'  ELSE
      "010"  WHEN R(2) = '1'  ELSE
      "001"  WHEN R(1) = '1'  ELSE
      "000" ;
  
```

--In this example,
Order is Important

--If NO request:

```
NO_REQ <= '1' WHEN R = "00000000" ELSE '0';
```

Concatenation operator:

$N \leftarrow D(0) \text{ \& } D(3 \text{ DOWNTO } 1);$

Example:

If $D = 1010$

then: $D(0) = 0$, $D(3 \text{ DOWNTO } 1) = 101$

Therefore: $N = 0 \text{ \& } 101 = 0101$

$M \leftarrow K(4 \text{ DOWNTO } 2) \text{ \& } L(3 \text{ DOWNTO } 1);$

Example:

If $K = 100101$ and $L = 001001$, then

$M = 001100$

Comparators

```
AGTB <= '1' WHEN A > B ELSE '0';
```

Other VHDL *relational* operators are as follows:

- Equal =
- Not equal /=
- Less than <
- Less than or equal to <=
- Greater than >
- Greater than or equal to >=

AGTB <= '1' WHEN A > B ELSE '0';

Logical and Relational operators may be combined:

GT <= '1' WHEN A1 > B1 AND B2 < A2 ELSE '0';

y <= '1' WHEN (a AND NOT b) = '1' ELSE '0';

z <= '1' WHEN a = '1' AND b = '0' ELSE '0';

y <= '1' WHEN ((a AND NOT b) = '1') AND (A1 < B1) ELSE '0';

Lab06 (Digitals I)

Behavioral Modeling of Digital Circuits

Conditional Signal Assignments


1. Two Textbooks and 8 Students

2. Min_Max

Objectives

- More frequently used digital circuits
- Conditional Signal Assignments in VHDL

 Hex to 7-segment Decoder and 7-segment Display



B and H are vectors.

Five more 7-segment displays on the DE1-Lite board:

HEX5 (leftmost), HEX4, HEX3, HEX2, HEX1

Package: (a .vhd file)

Holds component declarations:

Example:

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
PACKAGE dig1pack IS
```

```
    COMPONENT hex7seg
```

```
    PORT (  B      : IN      STD_LOGIC_VECTOR (3 DOWNT0 0);
```


```
           EN      : IN      STD_LOGIC;    -- Active-high enable input.
```

```
           H      : OUT     STD_LOGIC_VECTOR (6 DOWNT0 0)
```

```
    );
```

```
END COMPONENT;
```


```
END dig1pack;
```

 

Put this line in any file that uses the package:

USE work.dig1pack.all;

Two Textbooks and 8 Students

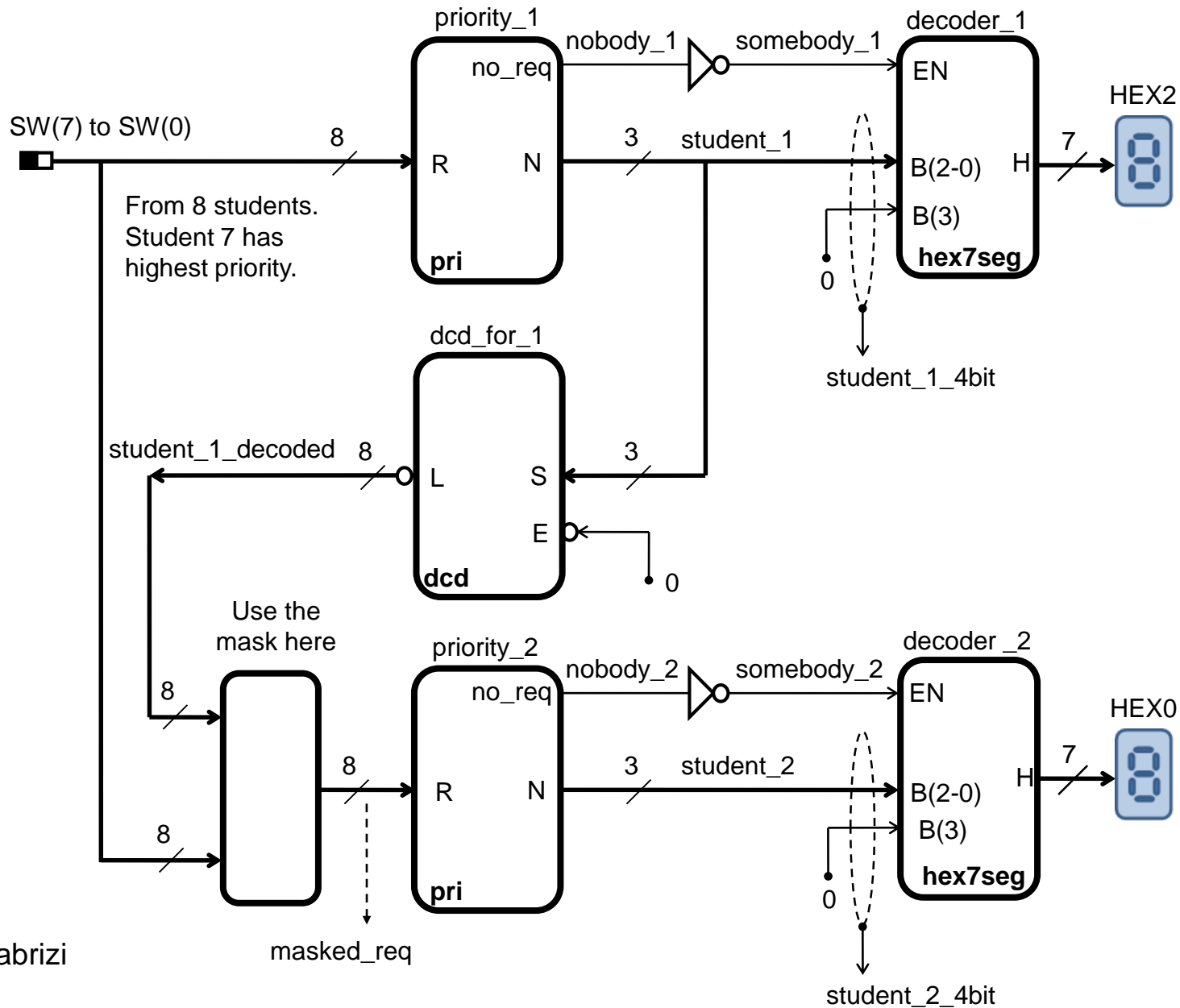

Chapter 5 - Part II


Behavioral Modeling of Digital Circuits

Conditional Signal Assignments
and

Selected Signal Assignments

N. Tabrizi


Kettering University

 

WITH **S** SELECT

```
M <=  A WHEN "00",  
      B WHEN "01",  
      C WHEN "10",  
      D WHEN OTHERS;
```

Selected Signal Assignment

 

WITH **S** SELECT

```
M <=  A WHEN "00",
      B WHEN "01",
      D WHEN OTHERS;
```

Selected Signal Assignment

Truth Tables

WITH **ST** SELECT

MJF <= '0' WHEN "000",
 '0' WHEN "001",
 '0' WHEN "010",
 '1' WHEN "011",
 '0' WHEN "100",
 '1' WHEN "101",
 '1' WHEN "110",
 '1' WHEN OTHERS;

Row	ST	MJF
0	0 0 0	0
1	0 0 1	0
2	0 1 0	0
3	0 1 1	1
4	1 0 0	0
5	1 0 1	1
6	1 1 0	1
7	1 1 1	1

Truth Tables

Shorthand

WITH **ST** SELECT

```
MJF <= '0' WHEN "000" | "001" | "010" | "100",  
        '1' WHEN OTHERS;
```

Row	ST	MJF
0	0 0 0	0
1	0 0 1	0
2	0 1 0	0
3	0 1 1	1
4	1 0 0	0
5	1 0 1	1
6	1 1 0	1
7	1 1 1	1

Lab 07 (Digitals I)
Behavioral Modeling of Digital Circuits
Selected Signal Assignments
Basic Arithmetic and Logic Unit (ALU)

Objectives

- Signed/Unsigned Addition/Subtraction/Comparison
- Selected Signal Assignments in VHDL

Arithmetic Logic Unit (ALU)

You design a simple ALU today.

ALU is a basic building block of Microprocessors.

So:


No ALU, No Microprocessor

No Microprocessor, No Computer

No Computer, No (Fill in the blank!)

From Lecture Slides, Chapter 5


Subtractor as Unsigned Comparator

 

How to generate Signed A less than B (SALB)?

Convert the unsigned comparator to a signed one

Method I

 

4-bit Signed Comparator

- | A | B |
|--------|----------------------|
| • 0111 | > 0101 (+7 > +5) |
| • 1100 | > 1001 (-4 > -7) |
| • 1111 | > 0011 (-1 > +3 NO!) |

Swap sign bits

Now unsigned comparator says:

- 0111 < 1011 (-1 < +3 Yes!) or

A < B

which is what a signed comparator should say.

Generate SALB Signal

Method 2 (we learn in this lab)

$A - B < 0$ (subtraction) means: $A < B$ (comparison)

So we need the sign of the difference, while OV is taken into consideration:


OV	MSb	Sign bit
0	0	0
0	1	1
1	0	1
1	1	0

Sign bit = OV XOR MSb

OV = Cin XOR Cout

Convert the unsigned comparator to a signed one

Method II

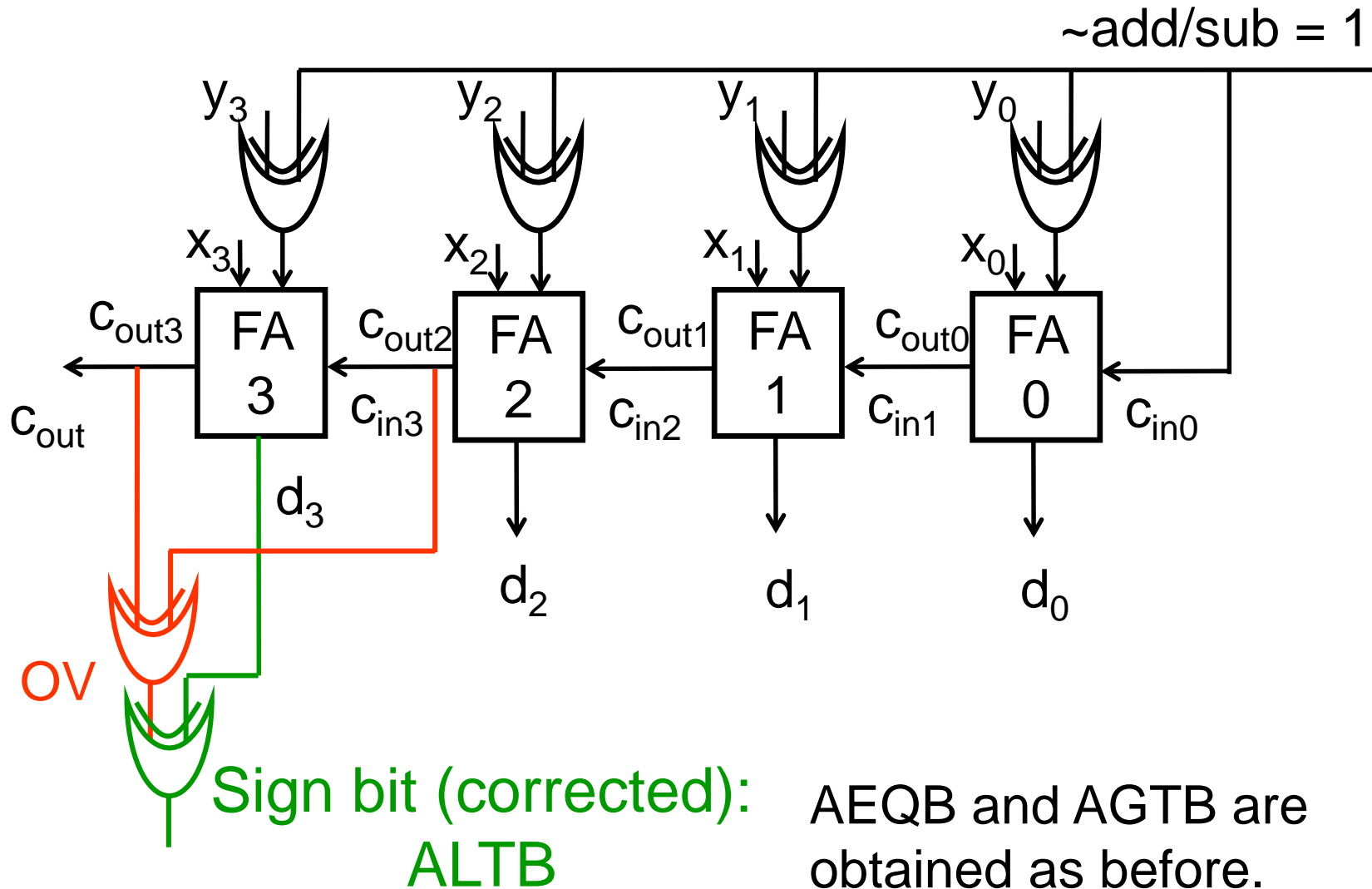


End of Chapter 5, Part II

More features

Concatenation operator:

Shorthand for repeated bits

 Example: extend the MSB to get a 32-bit vector from a 16-bit vector



```
data_32 <= (31 DOWNT0 16 => data_16(15)) & data_16;
```

Concatenation operator:

Shorthand for repeated bits

The assignment in the previous slide is equivalent to the following:

```
data_32 <=
data_16(15)&data_16(15)&data_16(15)&data_16(15)&
data_16(15)&data_16(15)&data_16(15)&data_16(15)&
data_16(15)&data_16(15)&data_16(15)&data_16(15)&
data_16(15)&data_16(15)&data_16(15)&data_16(15)&
data_16;
```

Use OTHERS to create a vector with repeated bits:

Example:

The following resets the whole vector to all zero:

```
zero16 <= (OTHERS => '0');
```

Use decimal instead of binary

```
use ieee.std_logic_1164.all;
```

```
use ieee.std_logic_arith.all;
```

```
conv_std_logic_vector(7, 9);
```

converts integer 7 to a std_logic_vector with 9 bits.

Example:

```
Z <= A WHEN m = '1' ELSE conv_std_logic_vector(0, 2);
```