



Digital Systems I

Instructor: Mohammad Ghamari


Electrical and Computer Engineering Department

Chapter 8


Design of Sequential Circuits (Finite State Machines)

Digital Circuits

(some well-known types)

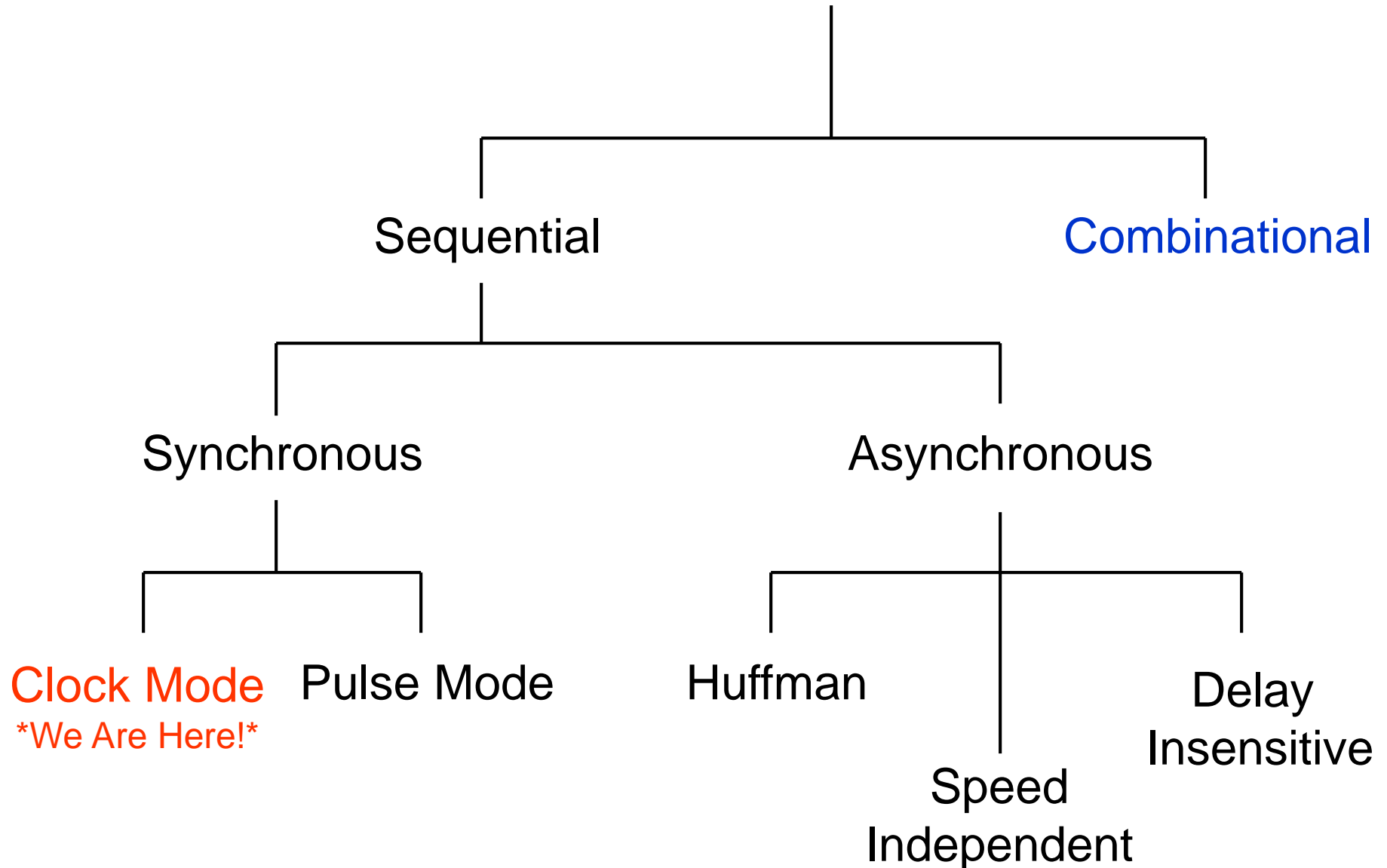

Problem (in natural language)

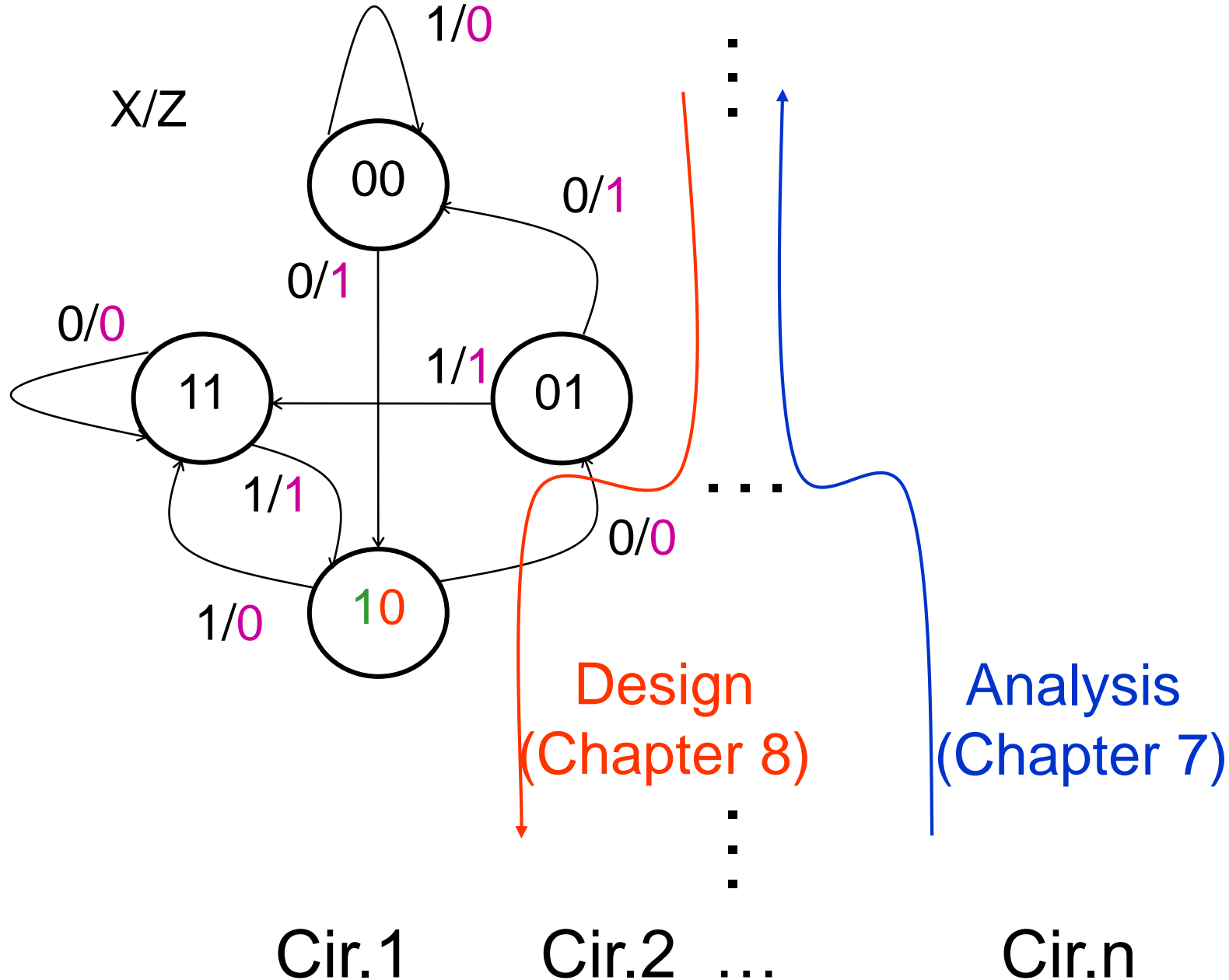


Good News 😊


Almost the same steps that we took in the analysis of FSMs, but in **reverse order**

Synchronous and Asynchronous signals

 Synchronous signal may only change with clock edges:





Asynchronous signal may change any time:

 

Synchronous and asynchronous signals

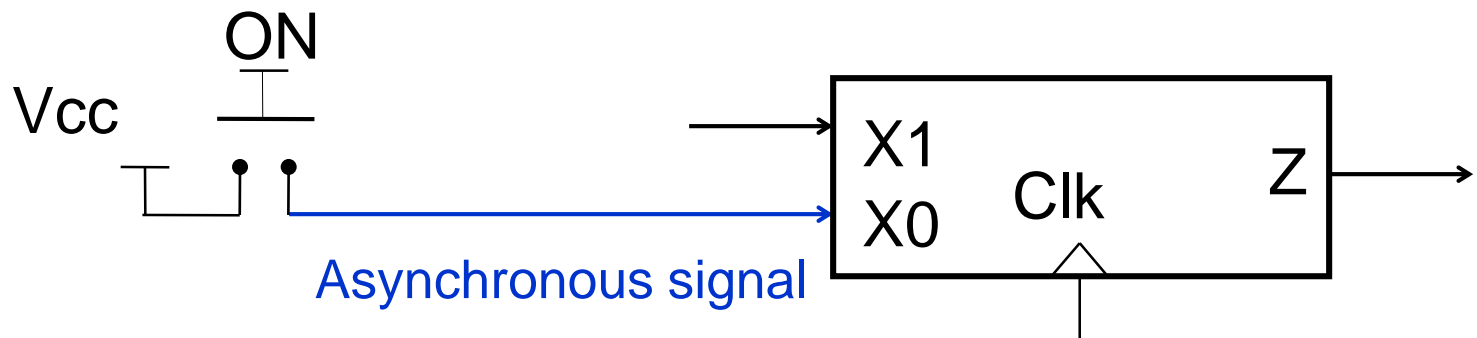 Synchronous signal is generated by a synchronous circuit with the same clock.



Design Steps

Step 1:

Translate natural language (word description) to state diagram

State machines Behavior

Can be observed in many devices in modern society **that perform a predetermined sequence of actions** depending on a **sequence of events with which they are presented**


- Vending Machines: which give products when the proper combination of coins is deposited
- Elevators: whose sequence of stops is determined by the floors requested by riders
- Traffic Lights, which change sequence when cars are waiting
- Combination Locks, which require the input of a sequence of numbers in the proper order




Cost of a bar of candy = 15¢



 Input N = $\begin{Bmatrix} 1 & 5\text{¢} \\ 0 & 0\text{¢} \end{Bmatrix}$



 
Input D = $\begin{Bmatrix} 1 & 10\text{¢} \\ 0 & 0\text{¢} \end{Bmatrix}$



Cost of a bar of candy = 15¢



 Input $N = \begin{cases} 1 & 5¢ \\ 0 & 0¢ \end{cases}$





Current State		Input	Next State		Output
Q1	Q0	Money In	Q'1	Q'0	Candy
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	0	0	1
1	1	0	0	0	1
1	1	1	0	0	1

Example 1. Develop a state diagram for the alarm control system of a chemical plant such that:

Starting with reset state ($P = 0$ & $T = 0$)

- If pressure goes up ($P = 1$) **after** temperature goes up ($T = 1$), alarm goes off while both P & T are high.
- Alarm turns off if P gets normal.
- Alarm turns on if P goes up again, while T is high.
- When T goes back to normal, above sequence repeats.

Timing Diagram

  


Same inputs ($T=1$, $P=1$) generate different outputs (alarm = **1** @ **t_0** but alarm = **0** @ **t_1**)

So we need a sequential circuit (FSM)

If pressure goes up ($P = 1$) **after** temperature goes up ($T = 1$), alarm goes off while both P & T are high.

State Diagram

 

While in **r** (as an example)


If **PT = 00** then go to **r**

If **PT = 10** then go to **w**

If **PT = 11** then go to **w**


If **PT = 01** then go to **a**

State Diagram: Output information added

 


 Example 7.

Add memory to a push-button; when button is pushed ($P = 1$) and then released ($P = 0$) an OFF light ($L = 0$) turns ON ($L = 1$) and remains ON until the button is pushed and released again.





Timing Diagram

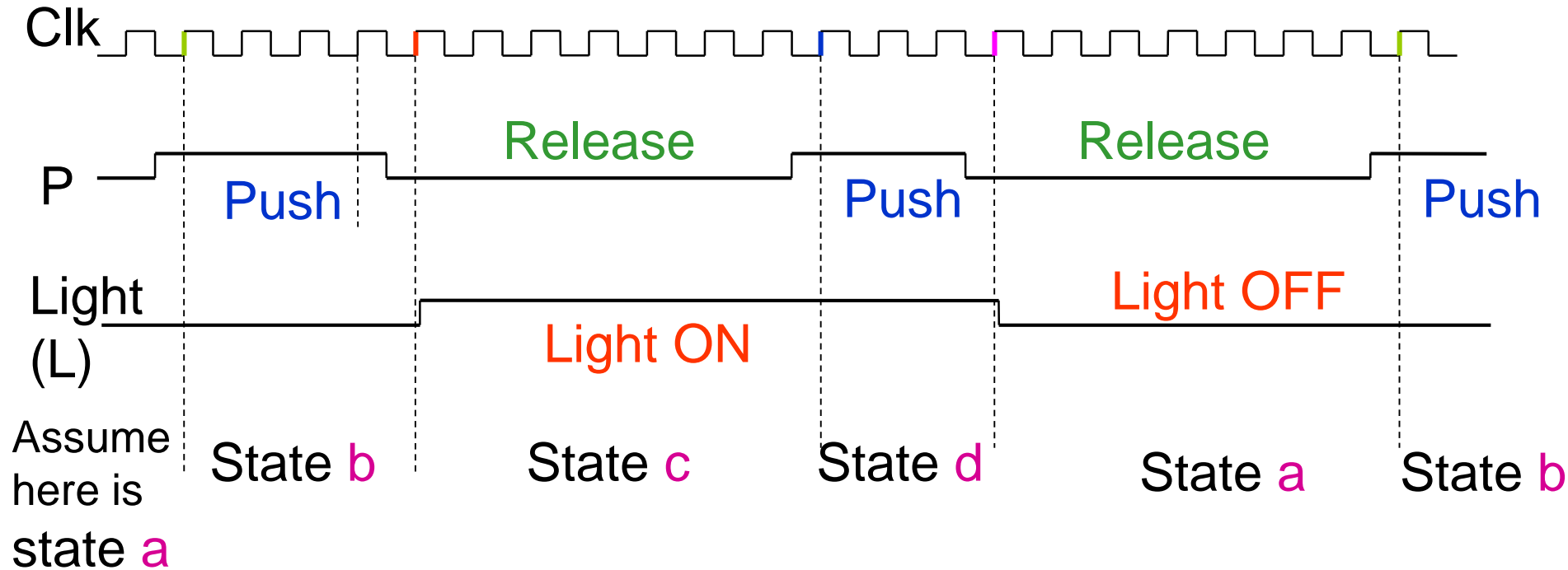

- With the first clock edge (after the button is pushed) the controller goes to state **b** (where the light is still off) and remains there until the button is released.
- The next clock edge takes controller to state **c**, where the light turns on.
- Again with the first clock edge (after the button is pushed) the controller goes to state **d** (where the light is still on) and remains there until the button is released.
- The next clock edge takes the controller to state **a**, where the light turns off again.

State Diagram

 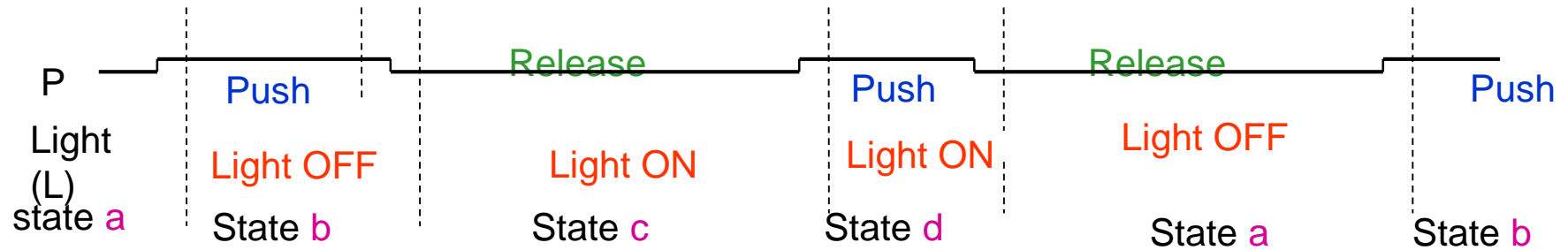

Finite State Machines (FSM)

Analysis:

Logic circuit


Excitation & output equations

Excitation & output maps

Partial transition tables

Transition table/graph

(State assignment, State graph)

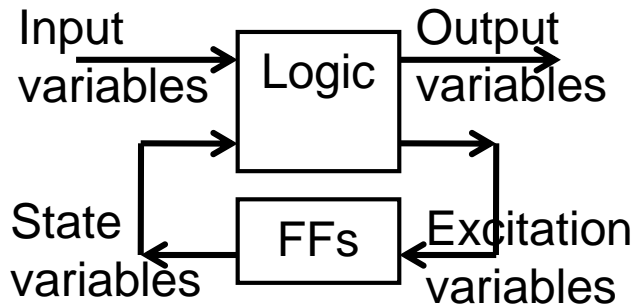

Design:

Natural language

State graph/state table

State minimization

State assignment, transition table

Partial transition tables

Excitation and output maps &

minimization

Excitation and output equations


Logic circuit

Design of Sequential Circuits

Steps 2 - 7

Example. Use D-FFs

1) State diagram (graph)

 


2) State table

Q	X	
	0	1
a	a, 0	c, 1
b	c, 1	a, 1
c	b, 0	a, 0

Q^{n+1}, Z

3) State minimization

 

Which one?

a or **e**

**Redundant states will
be identified and removed in this state**

4) State assignment & transition table

		X	
		0	1
Q1Q0	Q		
00	a	a, 0	c, 1
01	b	c, 1	a, 1
11	c	b, 0	a, 0
10			

Q^{n+1}, Z

		X	
		0	1
Q1Q0			
00		00, 0	11, 1
01		11, 1	00, 1
11		01, 0	00, 0
10		xx, x	xx, x

$Q1^{n+1} Q0^{n+1}, Z$

5) Partial transition tables

X	0	1
Q_1Q_0		
00	0	1
01	1	0
11	0	0
10	x	x

Q_1^{n+1}

X	0	1
Q_1Q_0		
00	0	1
01	1	0
11	1	0
10	x	x

Q_0^{n+1}

X	0	1
Q_1Q_0		
00	00, 0	11, 1
01	11, 1	00, 1
11	01, 0	00, 0
10	xx, x	xx, x

$Q_1^{n+1} Q_0^{n+1}, Z$

6) Choose FFs

- D-type is the least expensive
- Different types may result in different amounts of hardware to realize combinational circuits
- Different types may be used in the same design

7) Excitation & output maps and **minimizaion**

$$Q^{n+1} = D$$

Excitation maps = partial transition tables

X \ Q1Q0	0	1
00	0	1
01	1	0
11	0	0
10	x	x

D1

$$D1 = X.Q0' + X'.Q1'.Q0$$

X \ Q1Q0	0	1
00	0	1
01	1	0
11	1	0
10	x	x

D0

$$D0 = X.Q0' + X'.Q0$$

7) Excitation & output maps and minimizaion

		X	
		0	1
Q1Q0	00	0	1
	01	1	1
	11	0	0
	10	X	X


Z

$$Z = Q1'.Q0 + X.Q1'$$

 
7) Excitation & output maps and **minimizaion**

$$Q^{n+1} = D$$

Excitation maps = partial transition tables



 
$$D1 = (X + Q0) \cdot (X' + Q0') \cdot Q1'$$




$$D0 = (X + Q0) \cdot (X' + Q0')$$

 7) Excitation & output maps and minimizaion




$$Z = Q1' \cdot (X + Q0)$$

Finite-State Machines (Re-visited)

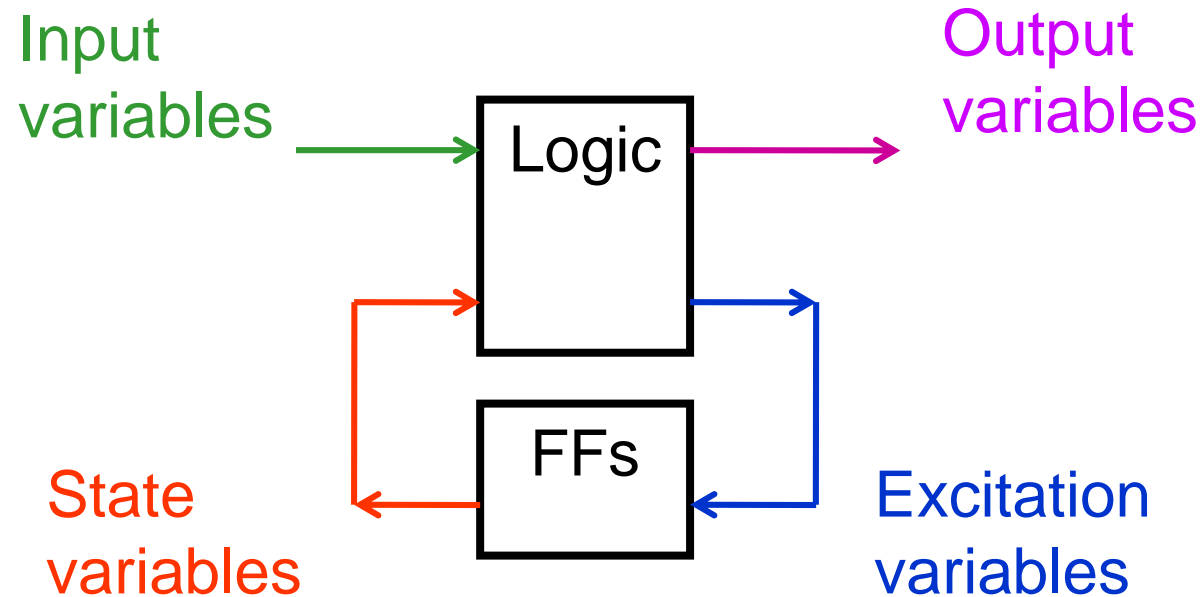

Example 9. Use D-FFs to realize the state diagram shown here.


1) State diagram (graph)

 

Try to solve this

Example 9. Use D-FFs

1) State diagram (graph)

 


2) State table

Q	X	
	0	1
a	c, 1	a, 0
b	a, 1	d, 1
d	d, 0	c, 1
c	b, 0	d, 0

Q^{n+1}, Z

3) State minimization

 

**Redundant states will
be identified here**

4) State assignment & transition table

		X	
		0	1
Q1Q0	Q		
00	a	c, 1	a, 0
01	b	a, 1	d, 1
11	d	d, 0	c, 1
10	c	b, 0	d, 0

Q^{n+1}, Z

		X	
		0	1
Q1Q0			
00		10, 1	00, 0
01		00, 1	11, 1
11		11, 0	10, 1
10		01, 0	11, 0

$Q1^{n+1} Q0^{n+1}, Z$

5) Partial transition tables

		X	
		0	1
Q1Q0	00	10, 1	00, 0
	01	00, 1	11, 1
	11	11, 0	10, 1
	10	01, 0	11, 0
		Q1 ⁿ⁺¹	Q0 ⁿ⁺¹ , Z

		X	
		0	1
Q1Q0	00	1	0
	01	0	1
	11	1	1
	10	0	1
		Q1 ⁿ⁺¹	

		X	
		0	1
Q1Q0	00	0	0
	01	0	1
	11	1	0
	10	1	1
		Q0 ⁿ⁺¹	

6) Choose FFs

- D-type is the least expensive
- Different types may result in different amounts of hardware to realize combinational circuits
- Different types may be used in the same design

7) Excitation & output maps and **minimizaion**

$$Q^{n+1} = D$$

Excitation maps = partial transition tables

Q1Q0	X	
	0	1
00	1	0
01	0	1
11	1	1
10	0	1

D1

$$D1 = X.Q1 + Q1.Q0 + X.Q0 + X'.Q1'.Q0'$$

Q1Q0	X	
	0	1
00	0	0
01	0	1
11	1	0
10	1	1

D0

$$D0 = X'.Q1 + Q1.Q0' + X.Q1'.Q0$$


7) Excitation & output maps and minimizaion

Q1Q0	X	0	1
00		1	0
01		1	1
11		0	1
10		0	0

Z


$$Z = X.Q0 + X'.Q1'$$

Circuit diagram

 


$$Z = X \cdot Q_0 + X' \cdot Q_1'$$

Circuit diagram

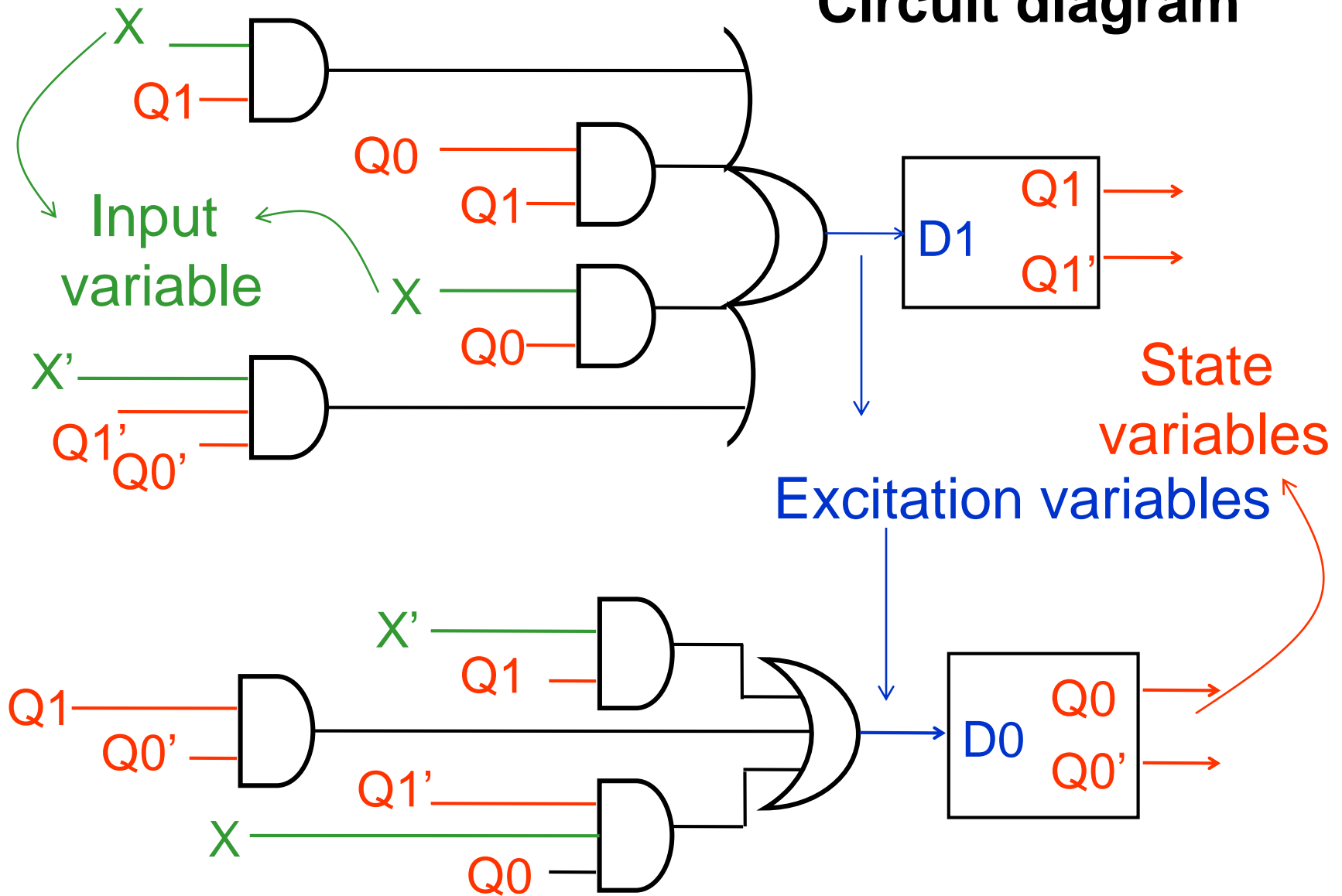


Design of synchronous circuits **using JK or T FFs** will not be covered, but you need to know what JK-FFs and T-FFs are and how they work.

Finite-State Machines (Re-visited)

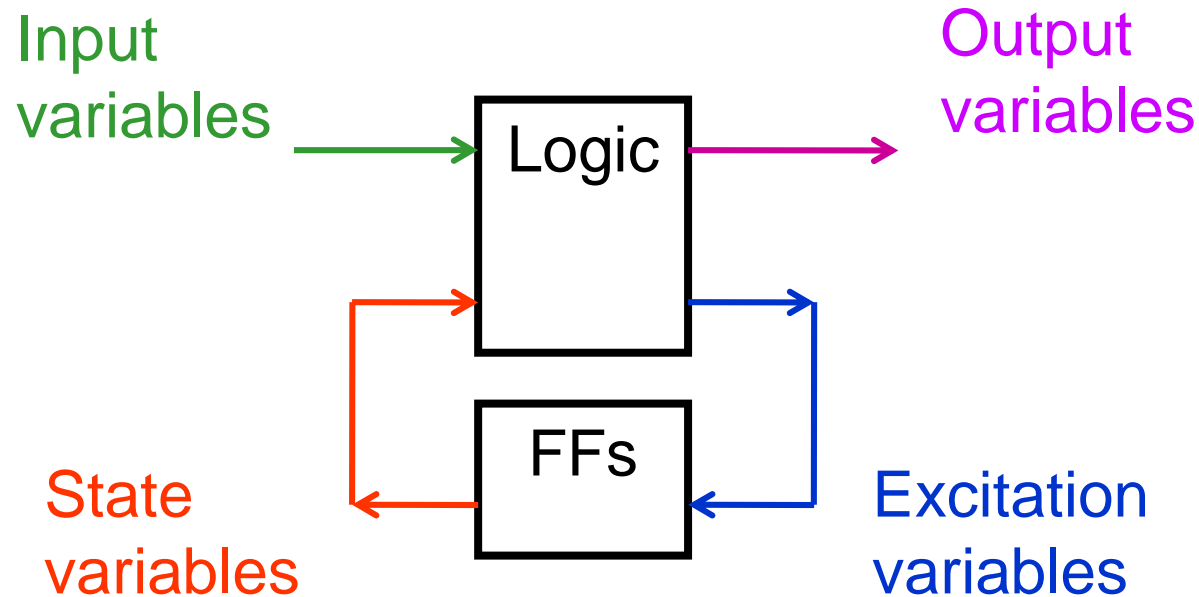


Mealy Machines

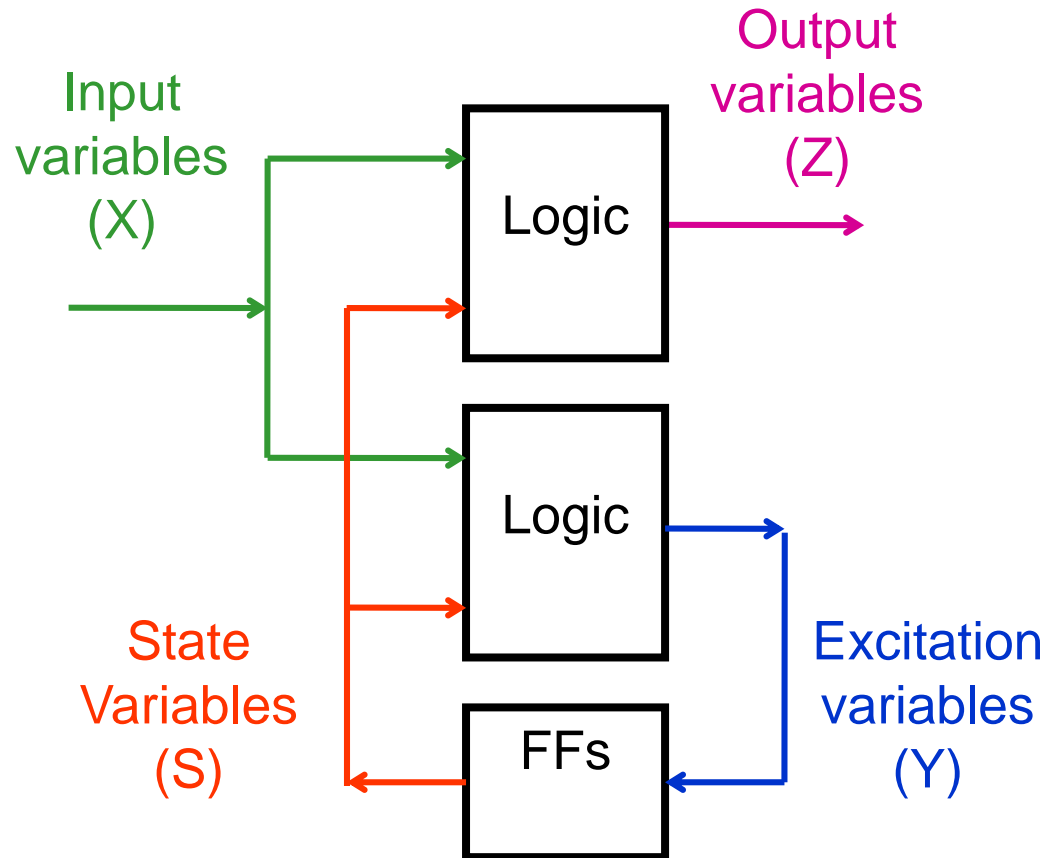Output is a function of state variables and inputs variables




Moore Machines

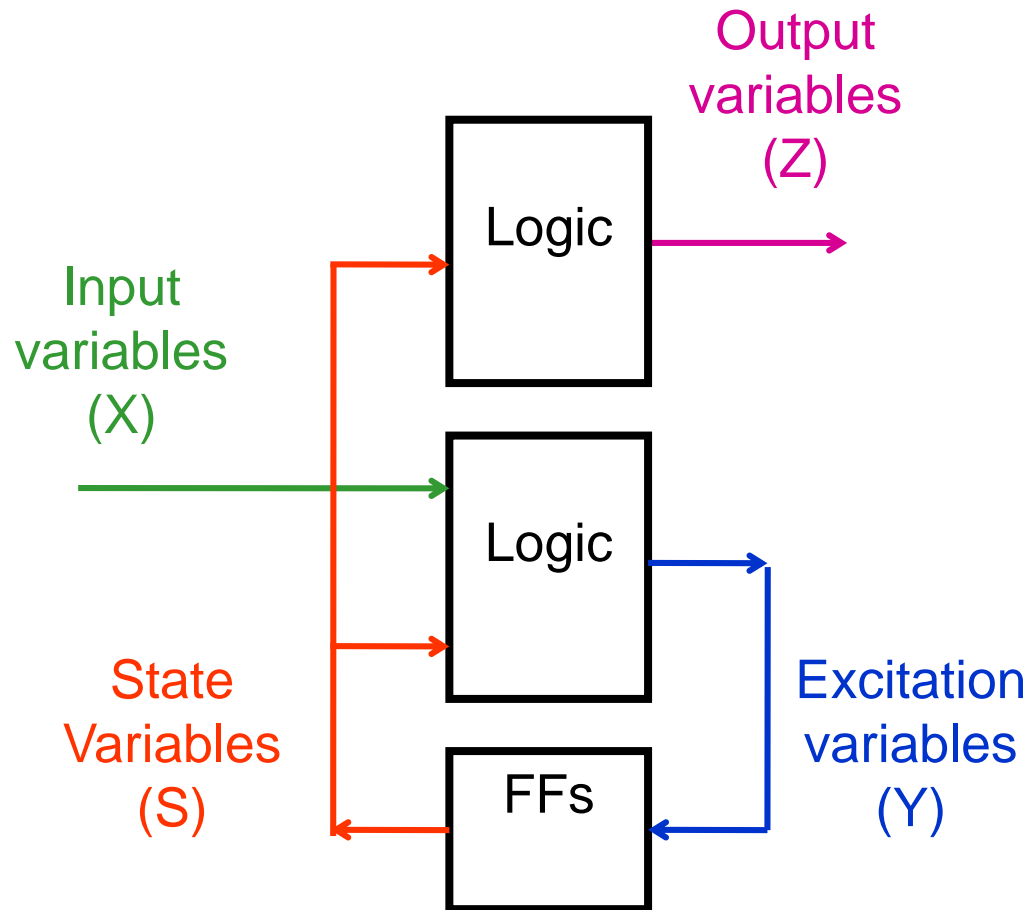Output is a function of state variables only.




Mealy Machine (Example)

 


Moore Machine (Example)


X/Z

 

Moore Machine (Example)

 


Mealy Machine (Example)

 

$$Z = X \cdot Q0 + X' \cdot Q1'$$

Moore Machine (Example)

 

$$Z = Q1 \cdot Q0 + Q1' \cdot Q0'$$

END