



Digital Systems I

Instructor: Mohammad Ghamari

Electrical and Computer Engineering Department

Chapter 4

Logic Minimization


Using Karnaugh Maps (K-map)

Example

Row	a b c	Y
0	0 0 0	1
1	0 0 1	0
2	0 1 0	0
3	0 1 1	1
4	1 0 0	0
5	1 0 1	0
6	1 1 0	0
7	1 1 1	1

What is Canonical SOP of this example?

Example

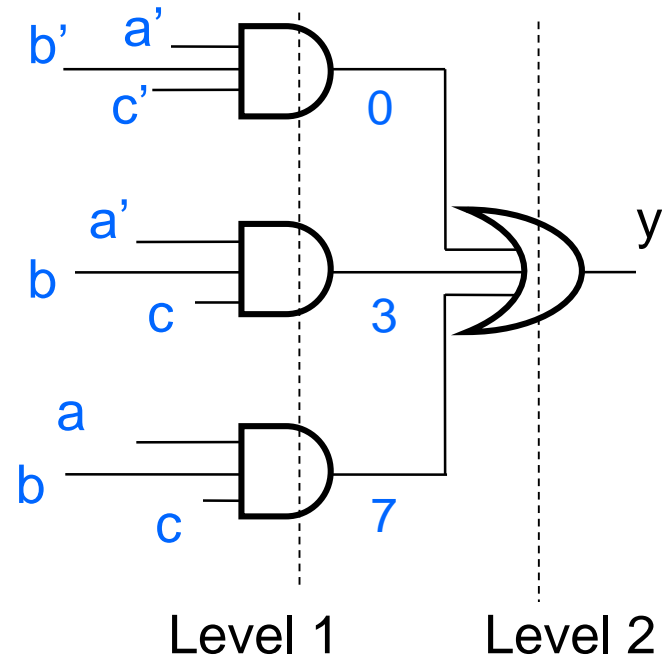


$$Y = \sum a, b, c \quad (0, 3, 7)$$

Canonical SOP: $Y = a' \cdot b' \cdot c' + a' \cdot b \cdot c + a \cdot b \cdot c$

Row	a b c	Y
0	0 0 0	1
1	0 0 1	0
2	0 1 0	0
3	0 1 1	1
4	1 0 0	0
5	1 0 1	0
6	1 1 0	0
7	1 1 1	1

Example

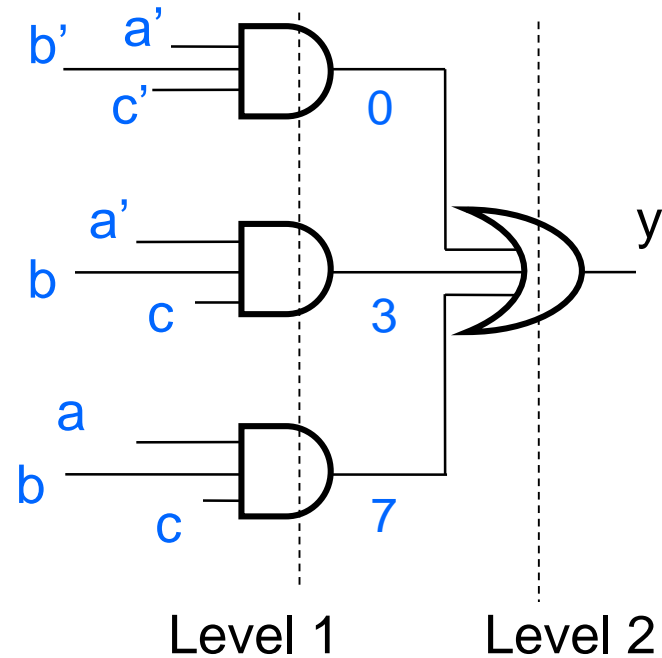



$$Y = \sum a, b, c \quad (0, 3, 7)$$

Canonical SOP: $Y = a' \cdot b' \cdot c' + a' \cdot b \cdot c + a \cdot b \cdot c$

Now please use switching algebra to simplify this circuit.

Row	a b c	Y
0	0 0 0	1
1	0 0 1	0
2	0 1 0	0
3	0 1 1	1
4	1 0 0	0
5	1 0 1	0
6	1 1 0	0
7	1 1 1	1

Example

 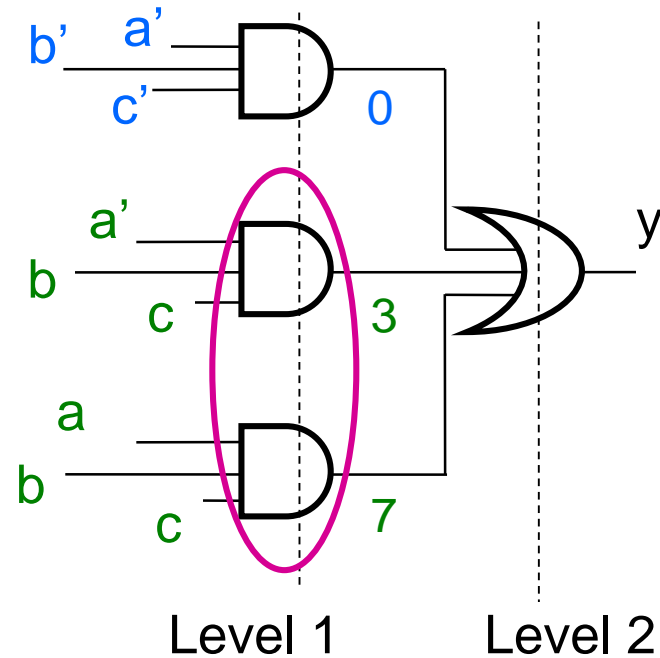

Row	a b c	Y
0	0 0 0	1
1	0 0 1	0
2	0 1 0	0
3	0 1 1	1
4	1 0 0	0
5	1 0 1	0
6	1 1 0	0
7	1 1 1	1

$$Y = \sum a, b, c \quad (0, 3, 7)$$

$$\text{Combining(T10): } a \cdot b + a \cdot b' = a$$


$$\text{Canonical SOP: } Y = a' \cdot b' \cdot c' + a' \cdot b \cdot c + a \cdot b \cdot c$$

$$\text{Combining theorem: } Y = a' \cdot b' \cdot c' + b \cdot c$$

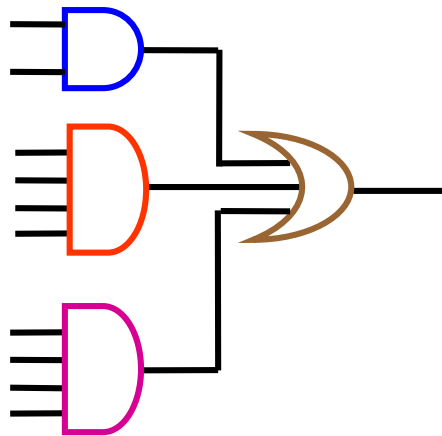Example from Chapter 3:


$$(a \cdot b) + (a \cdot b \cdot c' \cdot d) + (a \cdot b \cdot d \cdot e') = a \cdot b$$

Left side: 2-input AND 4-input AND 4-input AND
3-input OR



Left

Right side: 2-input AND

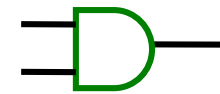

Right

Huge Difference!

How to simplify?

- **Switching algebra?**

Powerful & flexible, but

Not easy to apply manually.

- **Karnaugh maps, or K-maps** for short


A graphical representation for logic functions.

A two-dimensional version of truth table.

K-map-based procedure is able to obtain a *minimal* (2-level) SOP (& POS) for any switching function.


Problem (in natural language)

Truth table (or function)

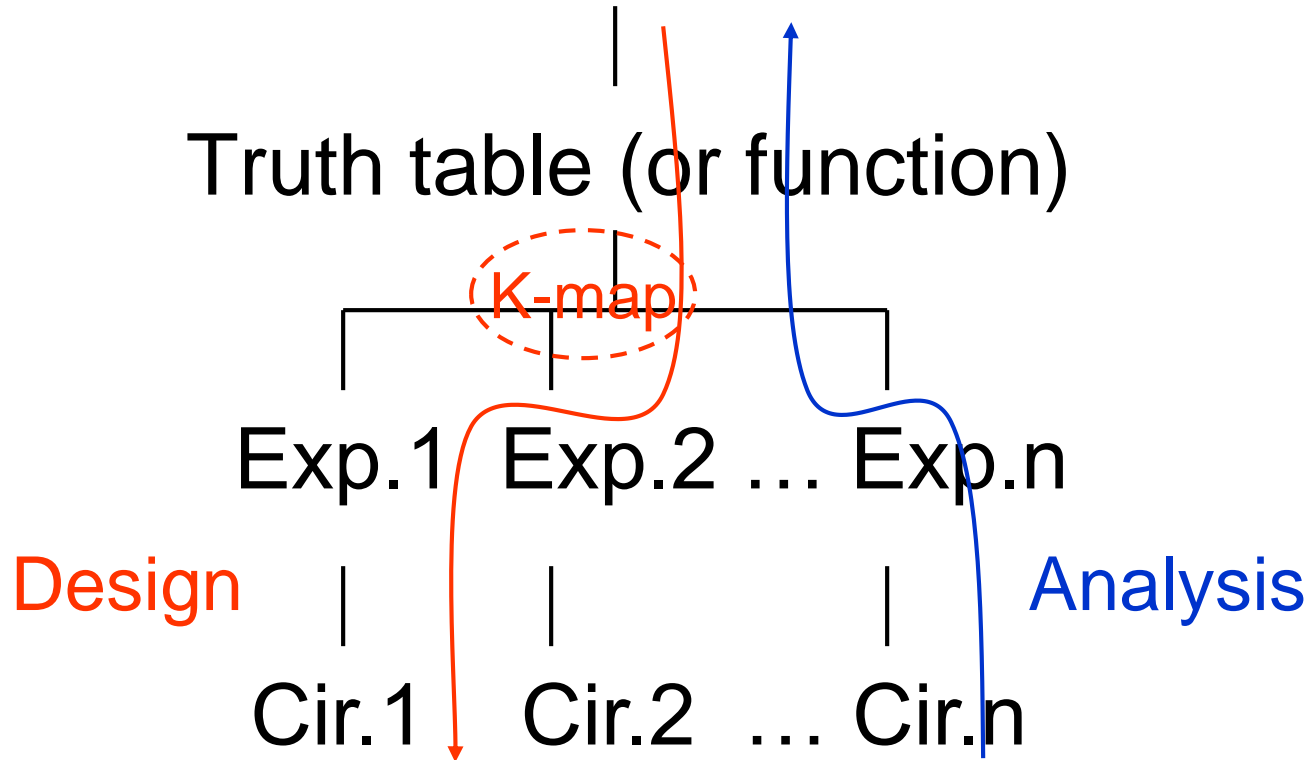


What is a 2-level logic?

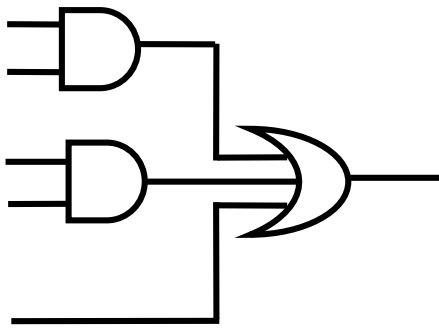
Each signal passes through 2 gates at the most to reach the output.



2-level

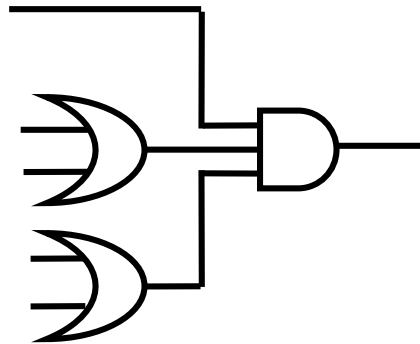

2-level

 


3-level

SOP and POS are 2-level logic


What is a minimal SOP?

By a minimal SOP we mean a SOP expression with as few product terms (AND terms) as possible.

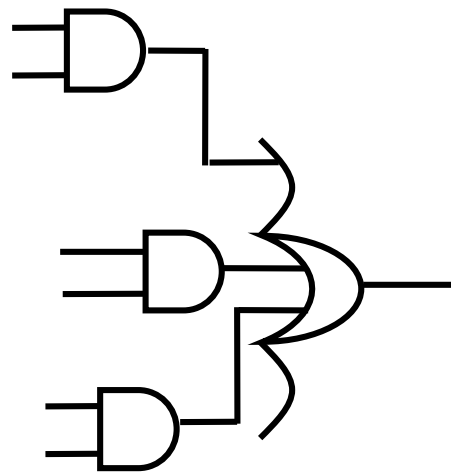If these are 2 choices, which one is minimal ?



Minimal

 


Not minimal

What is a minimal SOP? (Cont'd)


If there are 2 or more SOP expressions meeting this criterion, then the minimal SOP is the one with as **few literals** as possible.

If these are 2 choices, which one is minimal

Minimal SOP may not be unique.

 

Minimal

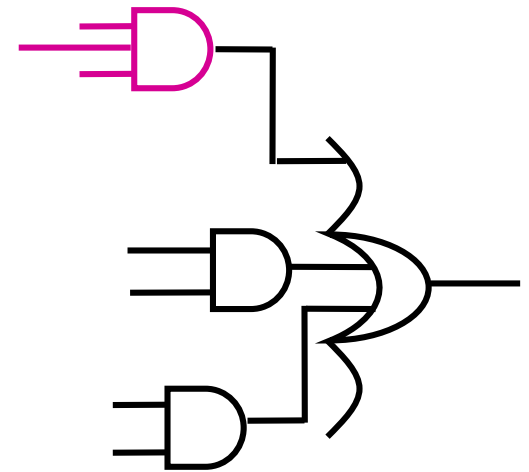

Not minimal

To avoid confusion, first consider minimal SOP.

Then concepts developed for SOP will easily be extended to POS.

K-maps: two-dimensional truth tables

		AB			
		00	01	11	10
C	0	0	2	6	4
	1	1	3	7	5

3-variable K-map

Row	ABC	Y
0	0 0 0	
1	0 0 1	
2	0 1 0	
3	0 1 1	
4	1 0 0	
5	1 0 1	
6	1 1 0	
7	1 1 1	

3-variable TT

Each box in K-map corresponds to one minterm

		AB			
		00	01	11	10
C	0	0 A'B'C'	2 A'BC'	6 ABC'	4 AB'C'
	1	1 A'B'C	3 A'BC	7 ABC	5 AB'C

3-variable K-map

Row	A B C	Minterm
0	0 0 0	A'B'C'
1	0 0 1	A'B'C
2	0 1 0	A'BC'
3	0 1 1	A'BC
4	1 0 0	AB'C'
5	1 0 1	AB'C
6	1 1 0	ABC'
7	1 1 1	ABC

3-variable TT

Transfer output column to K-map

		AB			
		00	01	11	10
C	0	0 ⁰ 1	2 ² 0	6 ⁶ 0	4 ⁴ 0
	1	1 ¹ 0	3 ³ 1	7 ⁷ 1	5 ⁵ 0

K-map representation

Cell 3: 1-cell or on-set cell

Cell 5: 0-cell or off-set cell

Row	ABC	Y
0	0 0 0	1
1	0 0 1	0
2	0 1 0	0
3	0 1 1	1
4	1 0 0	0
5	1 0 1	0
6	1 1 0	0
7	1 1 1	1

TT representation

2- & 4-variable K-maps

		A	
		0	1
B	0	0	2
	1	1	3

2-variable K-map

		AB			
		00	01	11	10
CD	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10

4-variable K-map

Look at horizontal & vertical **code words**

00, 01, 10, 11 Normal binary

00, 01, 11, 10 Gray code

AB					
CD		00	01	11	10
		0	4	12	8
00		0	4	12	8
01		1	5	13	9
11		3	7	15	11
10		2	6	14	10

Question 1.

What is the point in using **Gray code** in K-maps?

Wait ...

Definition (in K-map domain)

Two cells are *logically adjacent* if their coordinates are different in **exactly** one bit.

e.g. cells 6 & 14:

$ABCD = \textcircled{0}110$ & $ABCD = \textcircled{1}110$.

		AB			
		00	01	11	10
CD	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10

Definition (in algebraic domain)

Two minterms are logically adjacent if they differ in **only** one variable.

e.g. $(A') \cdot B \cdot C \cdot D'$ & $(A) \cdot B \cdot C \cdot D'$

Conclusion

Two minterms are logically adjacent if they belong to two logically adjacent cells and vice versa.

		AB			
		00	01	11	10
CD	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10

$A'BCD'$ $ABCD'$

Example 1. Use switching algebra to simplify

$$Y(A, B, C) = \sum(2, 6)$$

$$Y(A, B, C) = A' \cdot B \cdot C' + A \cdot B \cdot C'$$

Apply T10-L to the two product terms:

		AB			
		00	01	11	10
C	0	0 0	2 1 $A'BC'$	6 1 ABC'	4 0
	1	1 0	3 0	7 0	5 0

Combining

$$T10 \quad a \cdot b + a \cdot b' = a \qquad (a + b) \cdot (a + b') = a$$

$$Y = A' \cdot B \cdot C' + A \cdot B \cdot C' = B \cdot C'$$

Original circuit: two 3-input AND, one 2-input OR

Simplified circuit: one 2-input AND

Minterms $A' . B . C'$ & $A . B . C'$ are logically adjacent, because they differ in only one variable.

Conclusion

Two **logically adjacent** minterms, hence two **logically adjacent** 1-cells can be **combined** resulting in a simpler logic circuit.

Therefore

To **minimize** a logic circuit we need to identify all **logically adjacent** minterms or **logically adjacent 1-cells**.

Intermediate goal:

Identify all logically adjacent 1-cells.

Definition

Physically adjacent cells: 2 cells with 1 common side (edge)

		AB			
		00	01	11	10
CD	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10

		AB			
		00	01	11	10
CD	00	0	4	$AB C'D'$	8
	01	$A'B' C'D$	5	13	$AB' C'D$
	11	3	$A'B CD$	$AB CD$	11
	10	2	6	$AB CD'$	10

Assume

2 top & bottom sides are the same,
Also 2 right & left sides are the same.

Some examples

Question 1. (now we are ready to answer)

What is the point in using **Gray code** in K-maps?

00, 01, 10, 11 Normal binary

00, 01, 11, 10 Gray code

Answer 1. By using **Gray code**, *physically* adjacent cells become *logically* adjacent as well, and vice versa.

Question 2. Why is it important to make *physically adjacent* cells *logically adjacent* as well, and vice versa?

Answer 2.

Remember our intermediate goal:
Identify all logically adjacent 1-cells.

On the other hand,
Physically-adjacent 1-cells are
identified at a glance.

Therefore, logically adjacent
minterms are identified at a glance
as well.

**We have reached our intermediate
goal!**

		AB			
		00	01	11	10
CD	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10

Back to **Example 1**. $Y(A, B, C) = \Sigma(2, 6)$

Cells 2 and 6 are physically, hence logically adjacent

So the corresponding minterms ($A' \cdot B \cdot C'$, $A \cdot B \cdot C'$) can be combined.

A is different in 2 minterms, drop it; keep B & C' :

$$A' \cdot B \cdot C' + A \cdot B \cdot C' = B \cdot C'$$

		AB			
		00	01	11	10
C	0	0 0	2 $A'BC'$ 1	6 ABC' 1	4 0
	1	1 0	3 0	7 0	5 0

In Summary

Two adjacent minterms can be combined to produce one single *p-term* with *one variable fewer* than each minterm has.

To combine them, drop the only variable that appears as two different literals in the two minterms & keep the remaining literals.

$$A' \cdot B \cdot C' + A \cdot B \cdot C' = B \cdot C'$$

Example 2. (p. 6)

Use K-map to minimize $Y = \sum_{A, B, C} (2, 3)$.

Try to solve this