

Digital Systems I


Lab05 Slides based on **Chapter 4 - Part II**

**Hierarchical Designs
and
Structural Modeling**

N. Tabrizi


Kettering University

Single-bit partial Comparator

 

Single-bit partial Comparator

 
```
ENTITY comp_1 IS
PORT (A, B : IN  STD_LOGIC;
      Y : OUT STD_LOGIC
);
END comp_1;
```




Single-bit partial Comparator

```
ENTITY comp_1 IS
PORT (A, B : IN  STD_LOGIC;
      Y : OUT STD_LOGIC
);
END comp_1;
```

 
```
ARCHITECTURE Algebraic OF comp_1 IS
    SIGNAL T, U, W: STD_LOGIC;
BEGIN
    Y  <= W NAND U;
    W  <= B NAND T;
    U  <= A NAND T;
    T  <= A NAND B;
END Algebraic;
```



Symbol (Graphical Entity)

 


Component

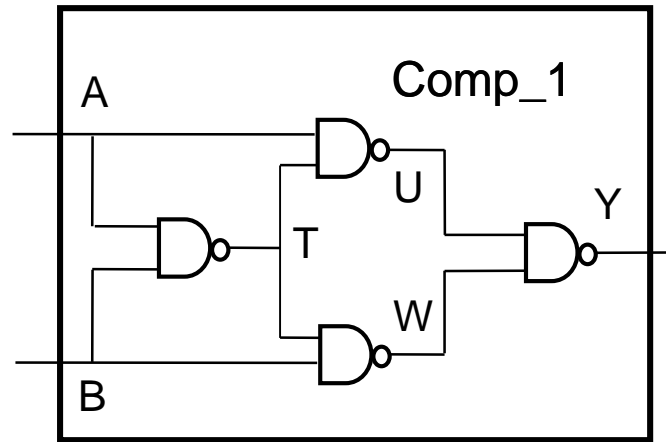

Definitions:

Component

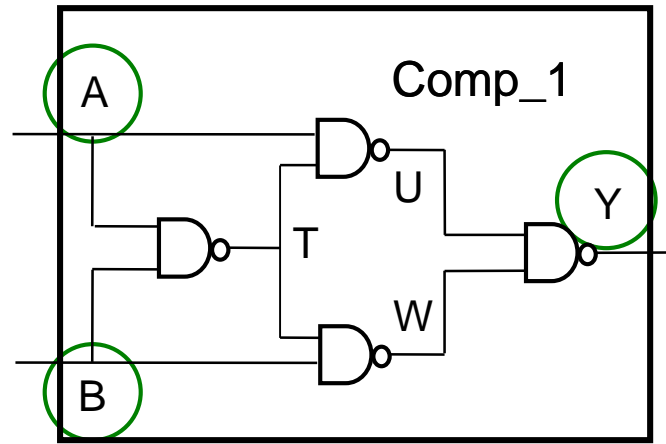

Why do we like
Components?

Because they are
REUSABLE

- **Formals:** Inputs/Outputs of component
- **Instantiate:** Copy and paste component into new design
- **Instance:** Resulting copy
- **Actuals:** Inputs/Outputs of instance (see next slide)

Structural Modeling

Shows how components are connected together

Structural Modeling


4-bit partial Comparator

First_Comparator: Instance Name

Com_1: Component Name

M(0), N(0), Z(0): Actuals

A, B, Y: Formals

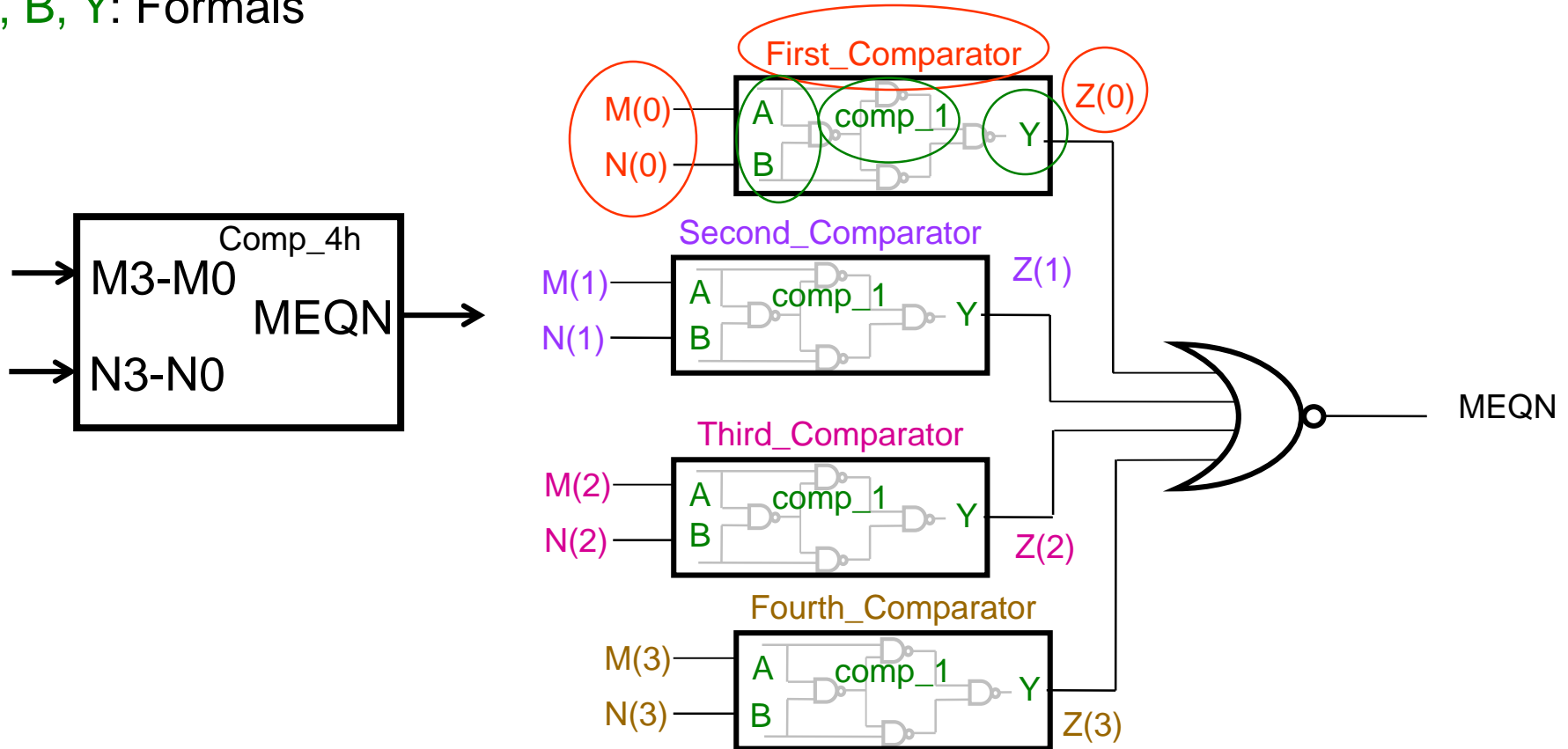

Structural Modeling

4-bit partial Comparator



```
ENTITY comp_4h IS
```

```
PORT (M, N : IN STD_LOGIC_VECTOR (3 DOWNT0 0);
```

```
      MEQN : OUT STD_LOGIC
```

```
);
```

```
END comp_4h;
```

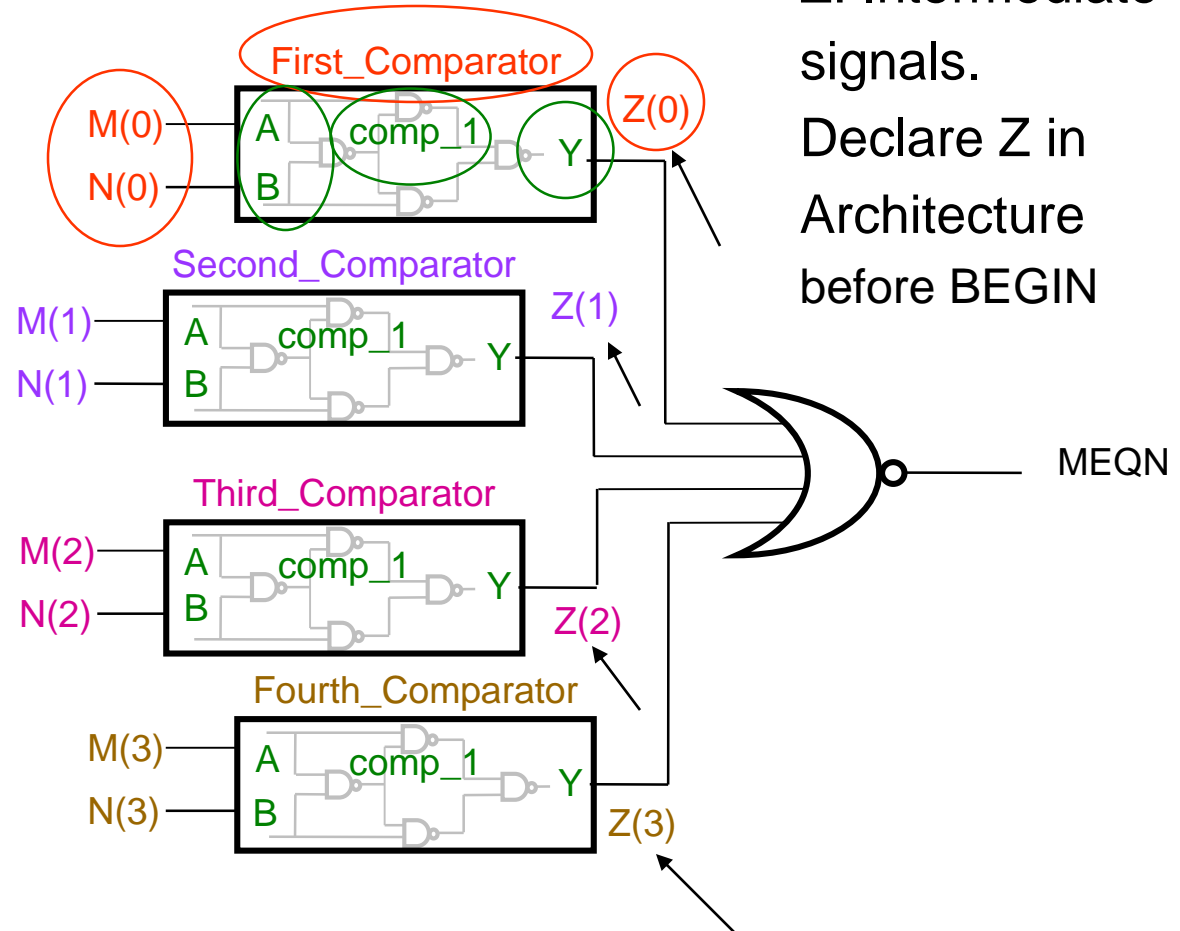 

ARCHITECTURE Structure OF comp_4h IS

COMPONENT comp_1

PORT (A, B: IN STD_LOGIC;
Y: OUT STD_LOGIC

END COMPONENT;

SIGNAL Z: STD_LOGIC_VECTOR (3 DOWNTO 0);


BEGIN

First_Comparator comp_1
PORT MAP (M(0), N(0), Z(0)); -- Actuals

END Structure;

NOTE: Add component declarations to ARCHITECTURE (See this page) Or put them in a separate file called a package (Coming up ...)

How to instantiate components:

 

NOTE: Write actuals in the same order that the formals are written.

How to instantiate components:

BEGIN

First_Comparator: comp_1

PORT MAP (M(0), N(0), Z(0));

Second_Comparator: comp_1

PORT MAP (M(1), N(1), Z(1));

Third_Comparator: comp_1


PORT MAP (M(2), N(2), Z(2));

Fourth_Comparator: comp_1


PORT MAP (M(3), N(3), Z(3));

MEQN <= NOT (Z(3) OR Z(2) OR Z(1) OR Z(0));


END Structure;

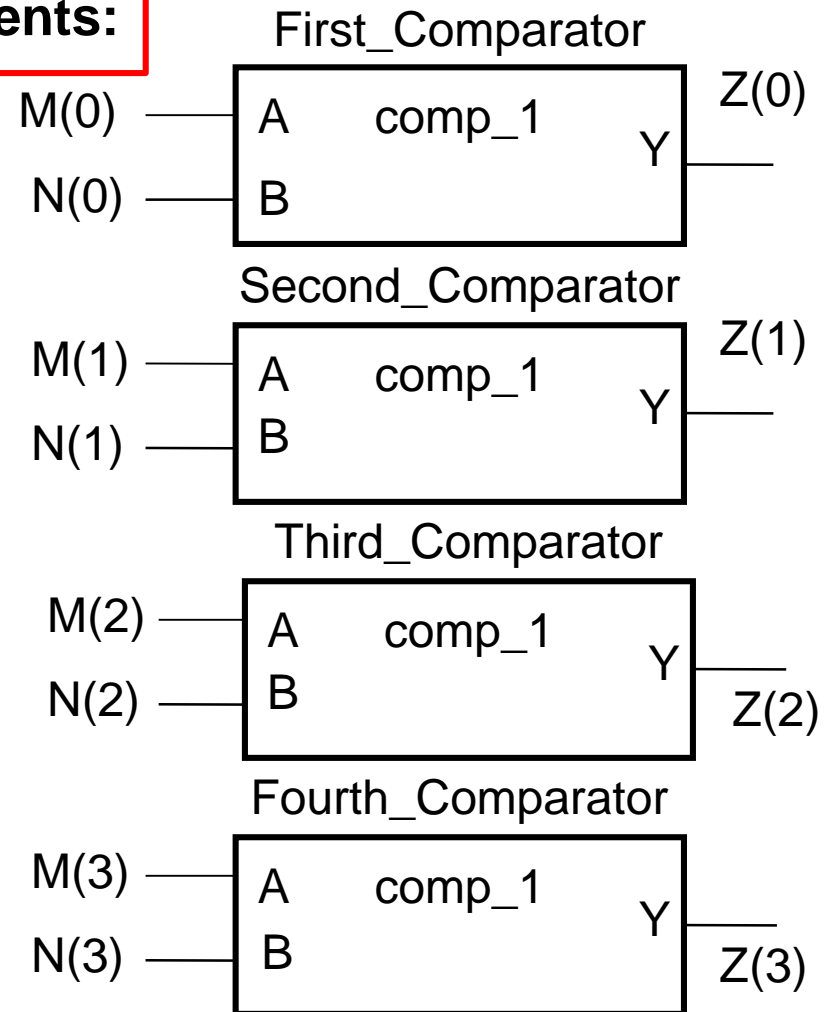

Note: NOR is added algebraically.

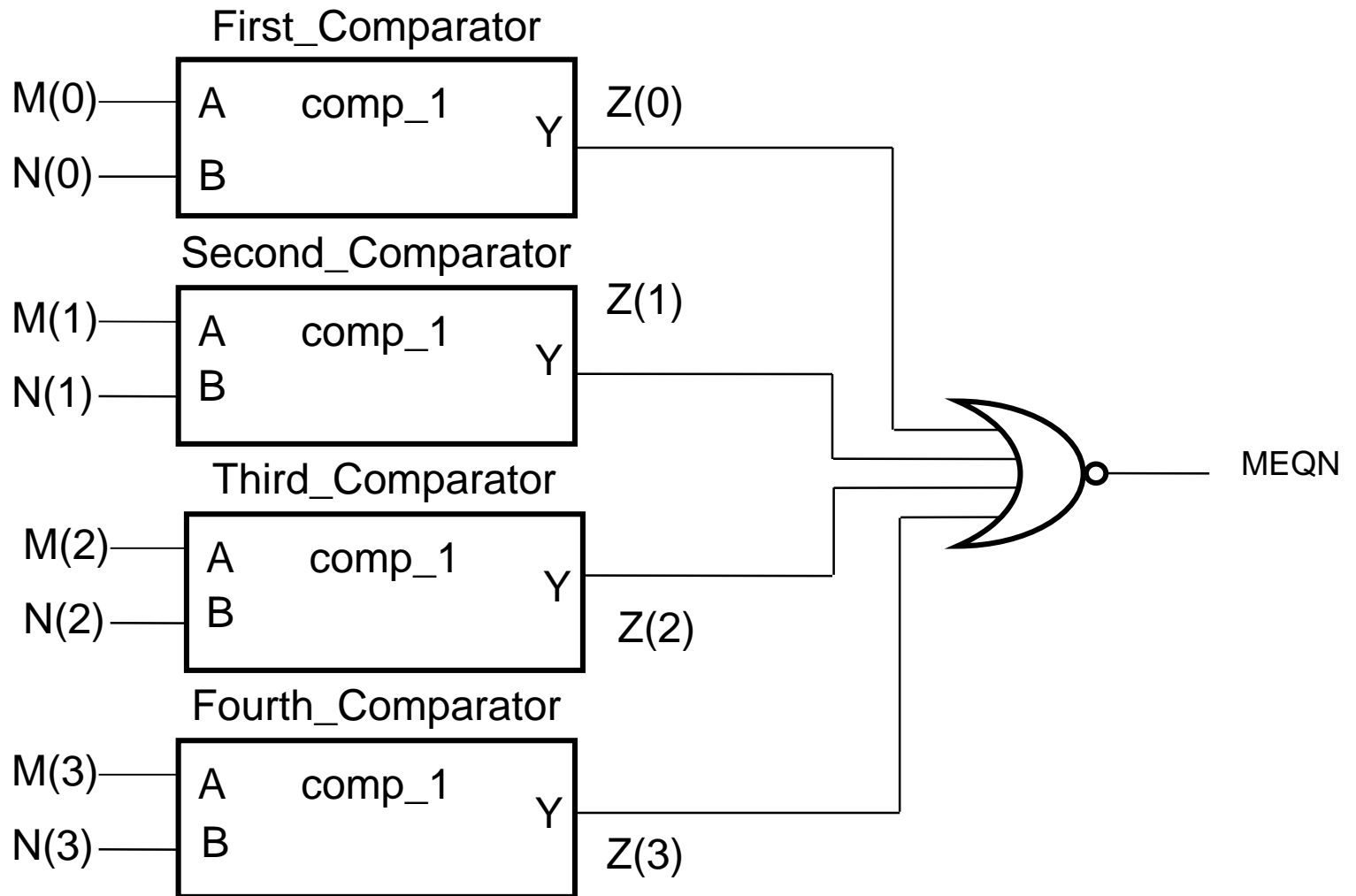

Note: NOR is added algebraically.

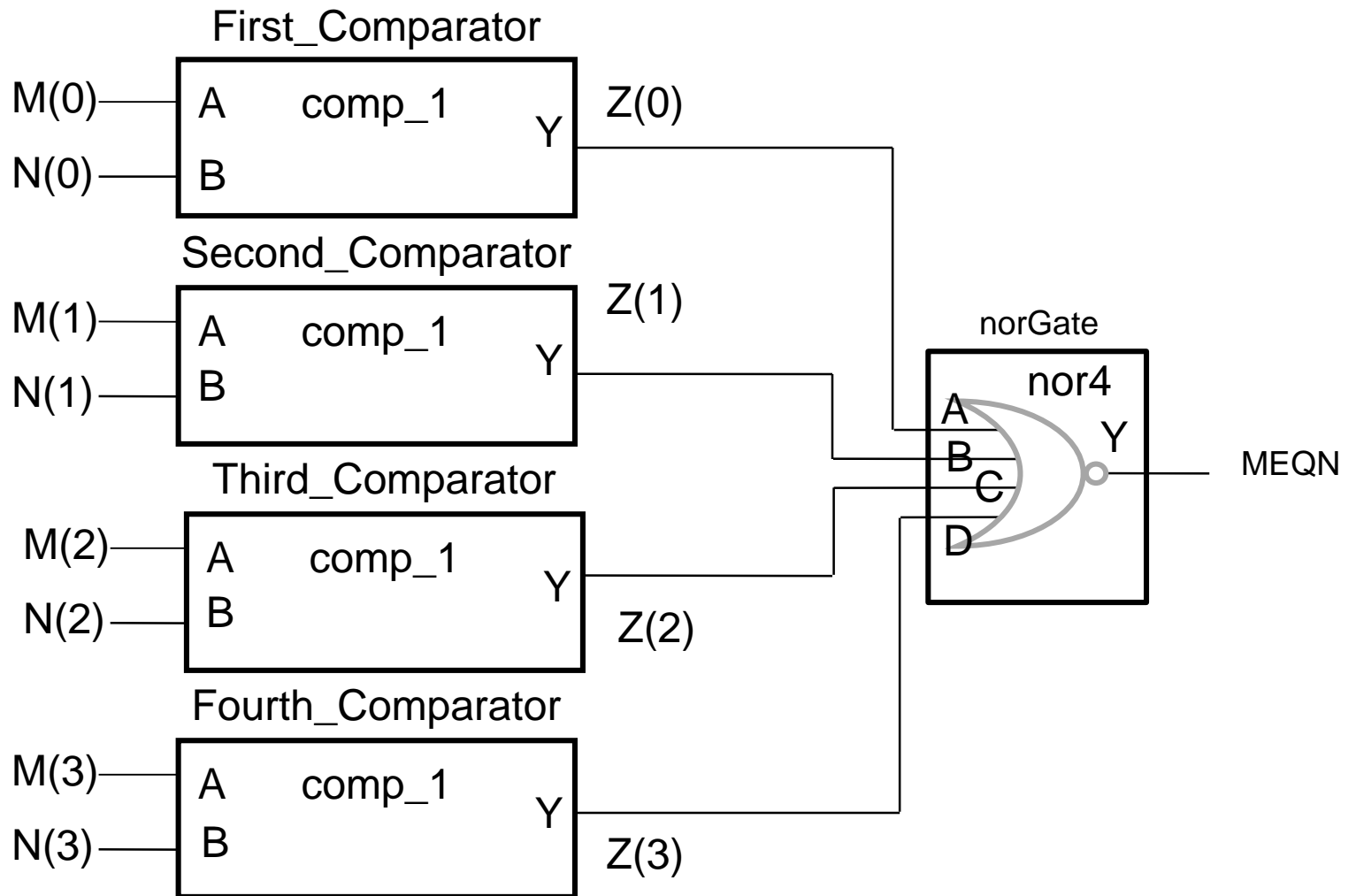

Note: NOR may also be added structurally instead of algebraically.

ARCHITECTURE Structure OF comp_4h IS

COMPONENT comp_1

PORT (A, B : IN STD_LOGIC;
Y : OUT STD_LOGIC
);

END COMPONENT;

COMPONENT nor4

PORT (A, B, C, D : IN STD_LOGIC;
Y : OUT STD_LOGIC
);

END COMPONENT;

SIGNAL Z: STD_LOGIC_VECTOR (3 DOWNT0 0);

Declare a new
component: nor4.

BEGIN

First_Comparator: comp_1

PORT MAP (M(0), N(0), Z(0));

Second_Comparator: comp_1

PORT MAP (M(1), N(1), Z(1));

Third_Comparator: comp_1

PORT MAP (M(2), N(2), Z(2));

Fourth_Comparator: comp_1


PORT MAP (M(3), N(3), Z(3));

norGate: nor4

PORT MAP (Z(0), Z(1), Z(2), Z(3), MEQN);

END Structure;

Instantiate nor4.

 

Now NOR is added structurally.

 

```
ENTITY nor4 IS
PORT (A, B, C, D : IN  STD_LOGIC;
      Y       : OUT STD_LOGIC
      );
END nor4;
```

Describe component
nor4

```
ARCHITECTURE algebraic OF nor4 IS
BEGIN
  Y <= NOT(A OR B OR C OR D);
END algebraic;
```

Lab05 Lecture Exercise


1.



What is the component's name?

What are the formals of the component?

Lab05 Lecture Exercise

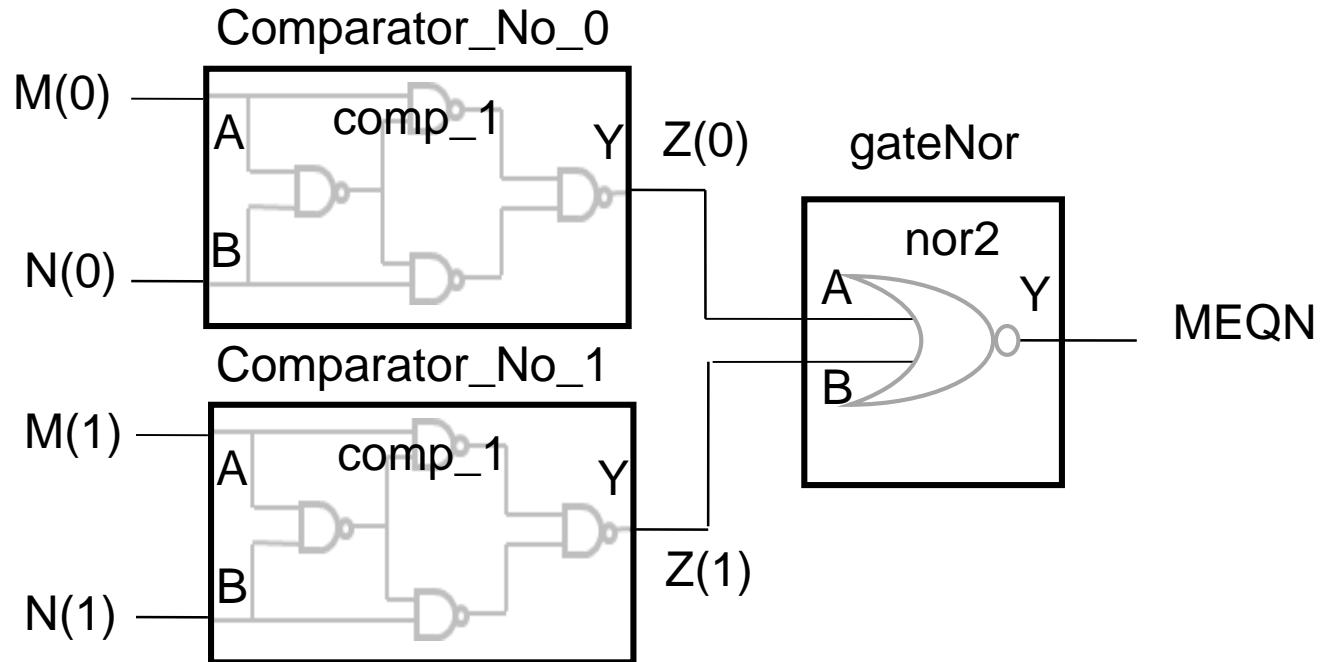

What is the name of first instance of `comp_1` (the one on top)?

Write the actuals of the second instance of `comp_1`:

A 4-bit partial comparator is here.

Convert it to a 2-bit comparator:

```
ENTITY comp_4h IS
```

```
PORT ( M, N : IN      STD_LOGIC_VECTOR (3 DOWNT0 0);  
      MEQN : OUT  STD_LOGIC    -- Active-high output  
      );
```

```
END comp_4h;
```

```
ARCHITECTURE Structure OF comp_4h IS
```

```
-- Intermediate signals
```

```
    SIGNAL Z: STD_LOGIC_VECTOR (3 DOWNT0 0);
```

```
    COMPONENT comp_1  -- Do NOT retype, copy/paste from ENTITY
```

```
    PORT (A, B : IN      STD_LOGIC;
```

```
          Y : OUT  STD_LOGIC
```

```
    );
```

```
END COMPONENT;
```

```

COMPONENT nor4
PORT (A, B, C, D : IN    STD_LOGIC;
      Y   : OUT  STD_LOGIC
    );
END COMPONENT;

BEGIN


    First_Comparator      : comp_1      PORT MAP
(M(0), N(0), Z(0));
    Second_Comparator      : comp_1 PORT MAP (M(1), N(1), Z(1));
    Third_Comparator       : comp_1 PORT MAP (M(2), N(2), Z(2));
    Fourth_Comparator      : comp_1 PORT MAP (M(3), N(3), Z(3));

    gateNor                 : nor4  PORT MAP(Z(3), Z(2), Z(1), Z(0), MEQN);
END Structure;

-- NOR gate is added structurally (not algebraically)
-- NOR gate needs its own file (entity and architecture) not shown here.
-- You need to compile ALL files when doing simulation or synthesis.

```

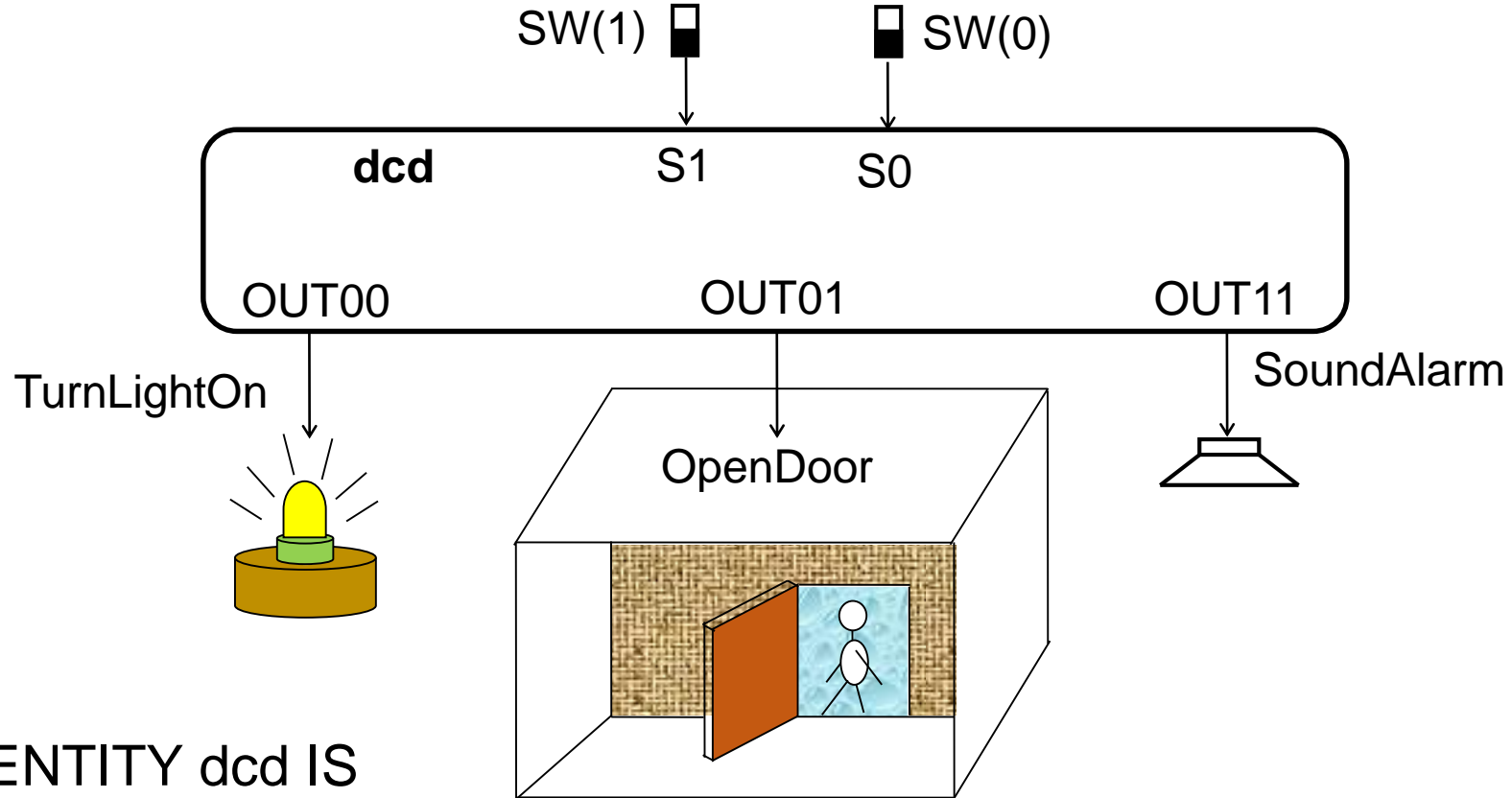2. Scott has built a control system, but when
He wants to open the door, the alarm sounds instead!
He tries to sound the alarm, the light turns on instead!
He wants to turn the light on, the door opens instead!



```

ENTITY dcd IS
PORT (
    s1, s0                : IN    STD_LOGIC;
    OUT00, OUT01, OUT11   : OUT   STD_LOGIC );
END dcd;


```

```

Controller: dcd    -- Controller is instantiated here
PORT MAP (SW(1), SW(0), OpenDoor, SoundAlarm TurnLightOn);

```

Hierarchical Design


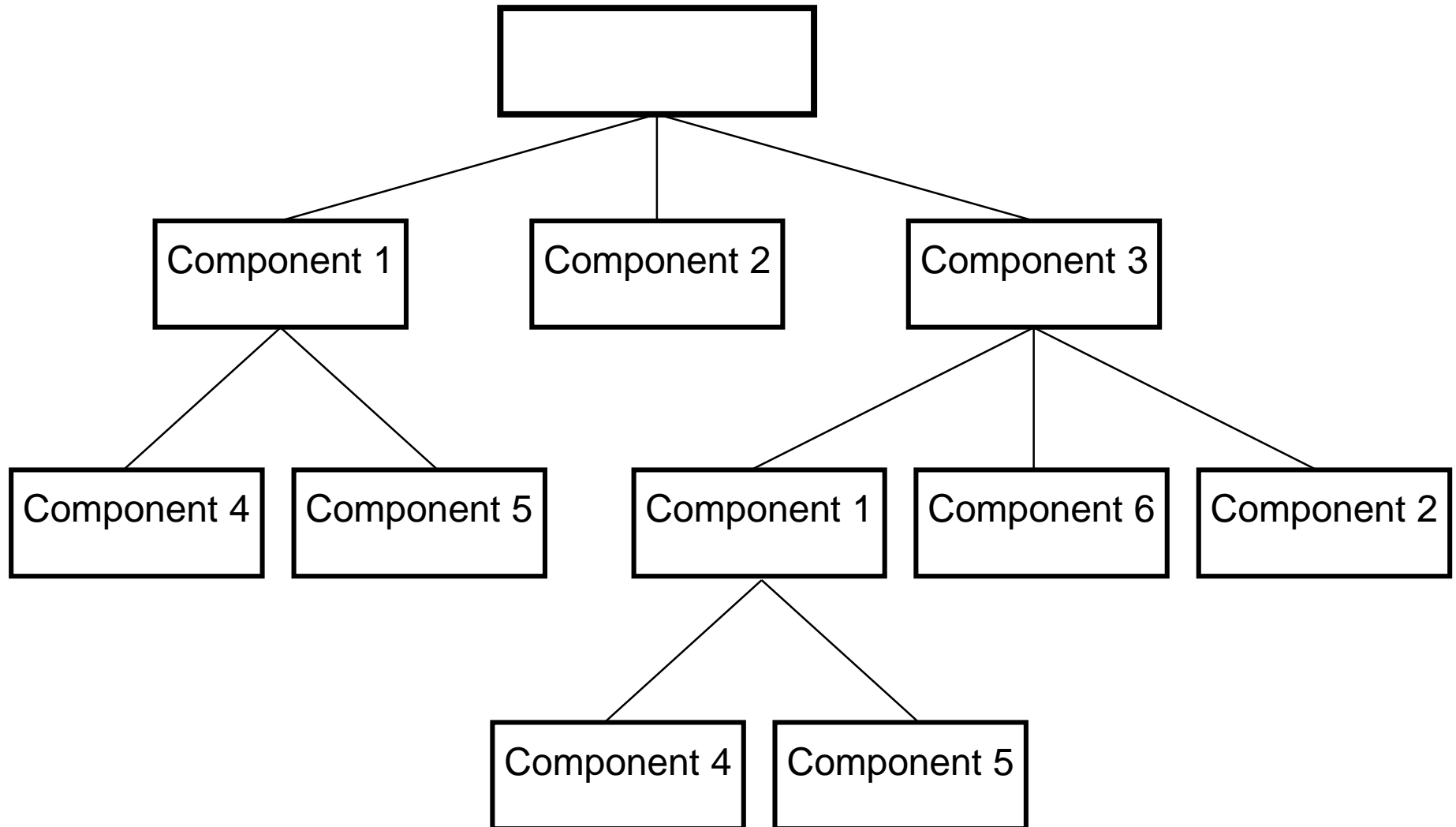



Preparing for lab05 of Digital Systems I

Multi-bit Full Comparator

Preparing for lab 05

Needs Your Close Attention

  

 

2-bit **Full** Comparator


Truth Table in Q17 of HW01

Row	A_1	A_0	B_1	B_0	GT	LT	EQ	Row	A_1	A_0	B_1	B_0	GT	LT	EQ
0	0	0	0	0	0	0	1	8	1	0	0	0	1	0	0
1	0	0	0	1	0	1	0	9	1	0	0	1	1	0	0
2	0	0	1	0	0	1	0	10	1	0	1	0	0	0	1
3	0	0	1	1	0	1	0	11	1	0	1	1	0	1	0
4	0	1	0	0	1	0	0	12	1	1	0	0	1	0	0
5	0	1	0	1	0	0	1	13	1	1	0	1	1	0	0
6	0	1	1	0	0	1	0	14	1	1	1	0	1	0	0
7	0	1	1	1	0	1	0	15	1	1	1	1	0	0	1


Pre-lab: Draw K-maps. Get minimal SOP & POS


Use **2-bit comparator** slices to get an **8-bit comparator**

What we have

 


What we need

 

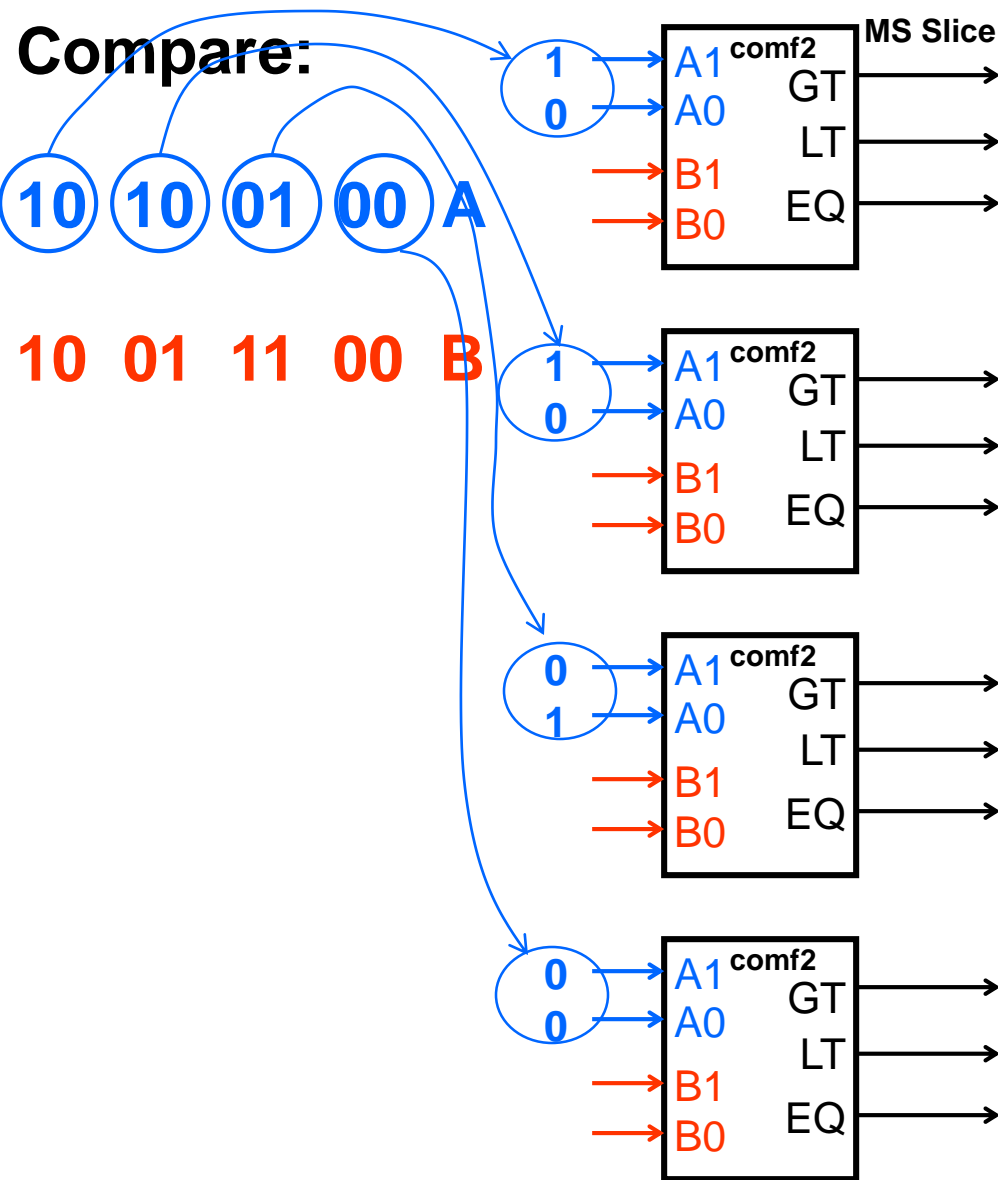


Compare:



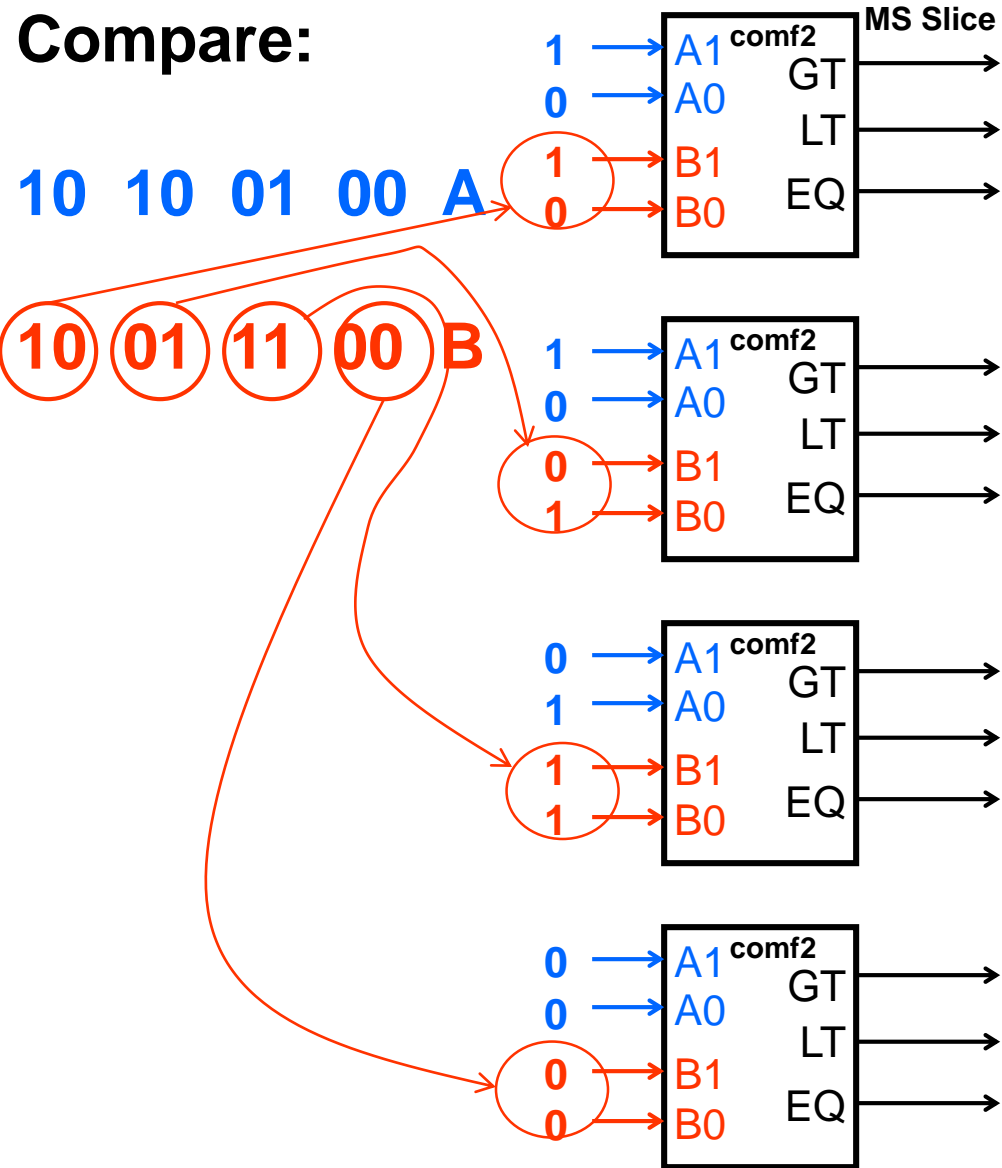


Compare:

10 10 01 00 A

 


10 01 11 00 B

 
 
 


Compare:

10 10 01 00 A
10 01 11 00 B

 


   In my stage **A = B**
Give this message to lower stage




Compare:

10 10 01 00 A
10 01 11 00 B

 

In my stage **A = B**



Give this message to lower stage

 

In my stage **A > B**


This is final message.

Give it to lower stage.

  


Compare:


10 10 01 00 A
10 01 11 00 B

 

 
In my stage **A = B**
Give this message to lower stage



 In my stage **A > B**
This is final message.
Give it to lower stage.




 In my stage **A < B**
But tell next stage **A > B**




Compare:


10 10 01 00 A
10 01 11 00 B

 

 
In my stage **A = B**
Give this message to lower stage



 In my stage **A > B**
This is final message.
Give it to lower stage.



 In my stage **A < B**
But tell next stage **A > B**




In my stage **A = B**
But final message is **A > B**

Compare:

10 10 01 00 **A**


10 01 11 00 **B**

What is the
FINAL
Decision?

 

In my stage **A = B**


Give this message to lower stage

 

In my stage **A > B**


This is final message.

Give it to lower stage.

 

In my stage **A < B**

But tell next stage **A > B**

 

In my stage **A = B**
But final message is **A > B**

Final decision: **A > B**

Definition:

A **message** tells us whether $A > B$, $A < B$ or $A = B$

Conclusion:

Each stage receives 2 messages:

One from its own comparator, one from upper level

And sends one of them to the lower level using these rules:

1. If more significant stage tells you $A > B$ or $A < B$, listen to it, no matter what your comparator says.
2. If the more significant stage tells you $A = B$, listen to your comparator.

Replace English Conversation with an Electronic Conversation!

Replace English Conversation with an Electronic Conversation!

New component: ei (**E**xpansion **I**nterface)


Replace English Conversation with an Electronic Conversation!


New component: ei (**E**xpansion **I**nterface)


Definition:

A **message** is a 3-bit Vector: $A > B$, $A < B$, $A = B$



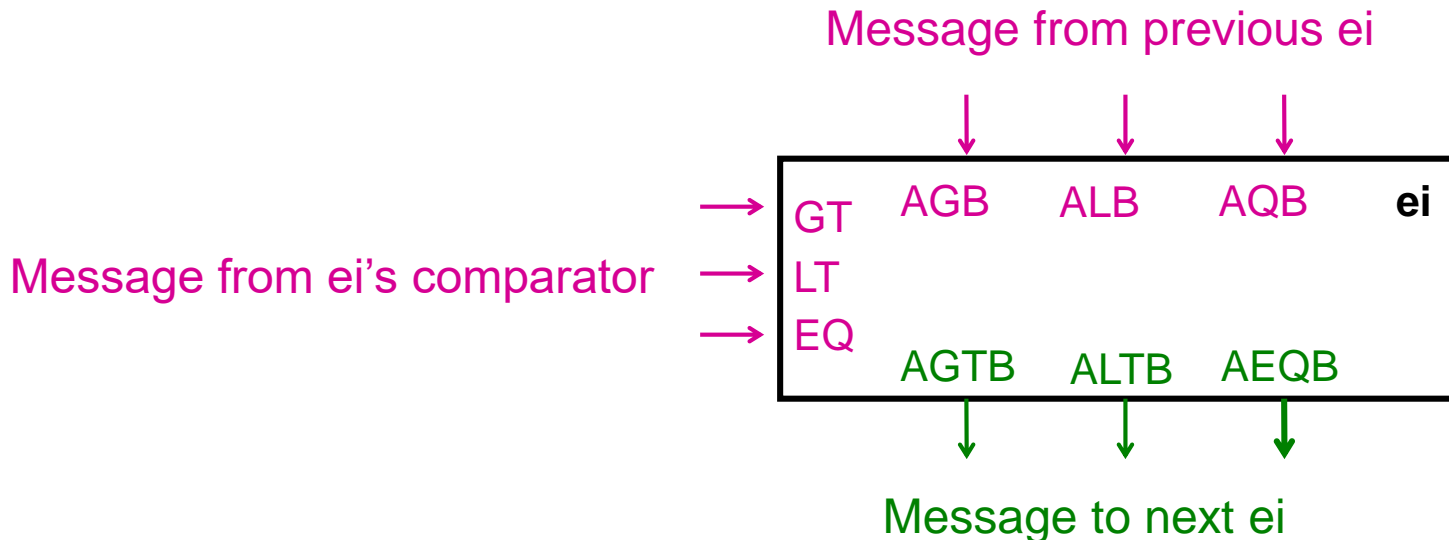
ei receives 2 messages and generates 1 message:




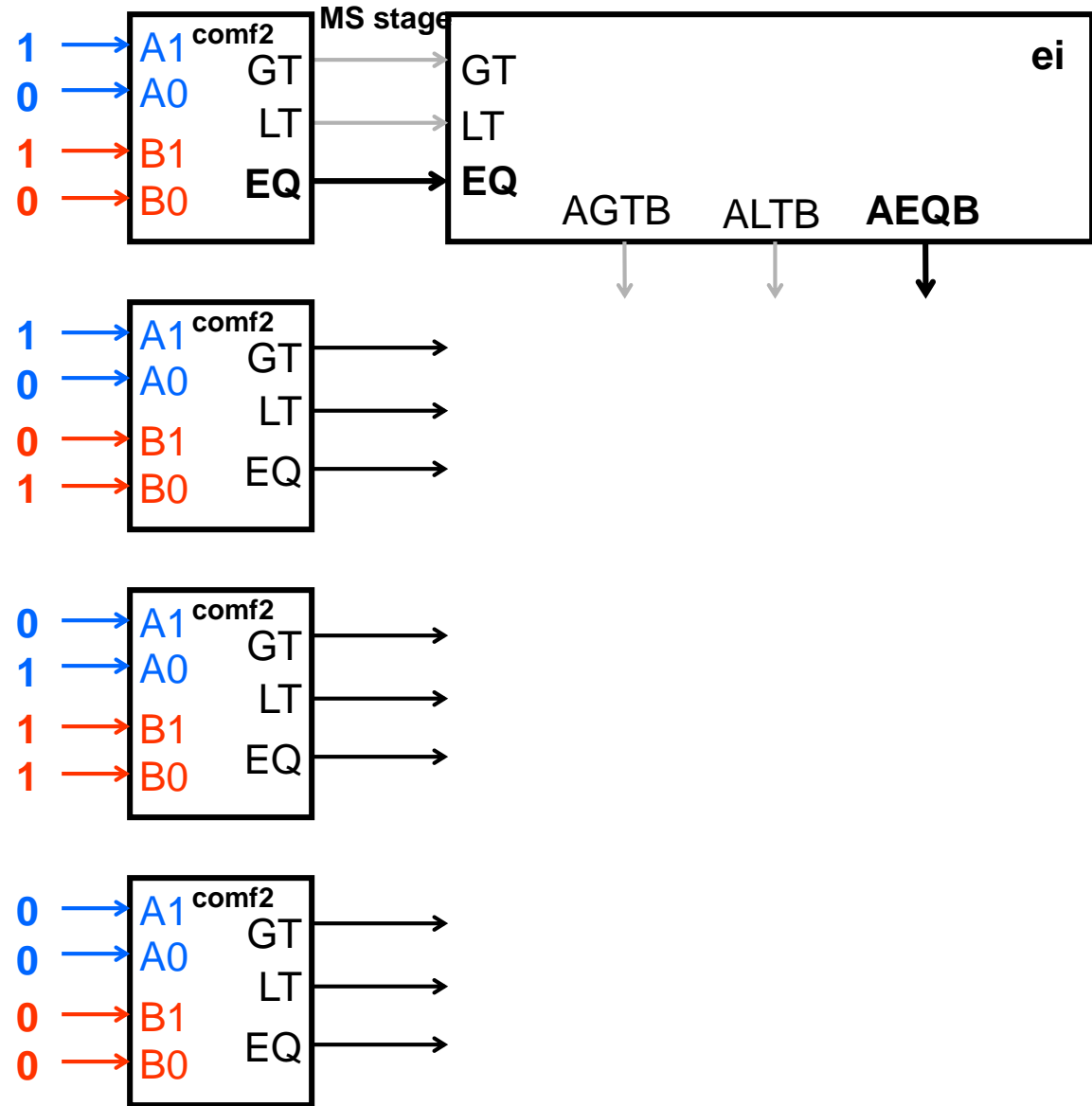

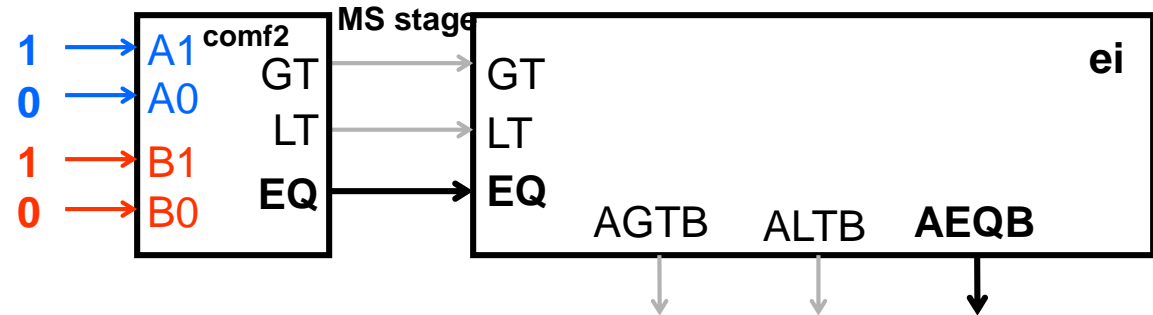



Listen to your
comparator

   


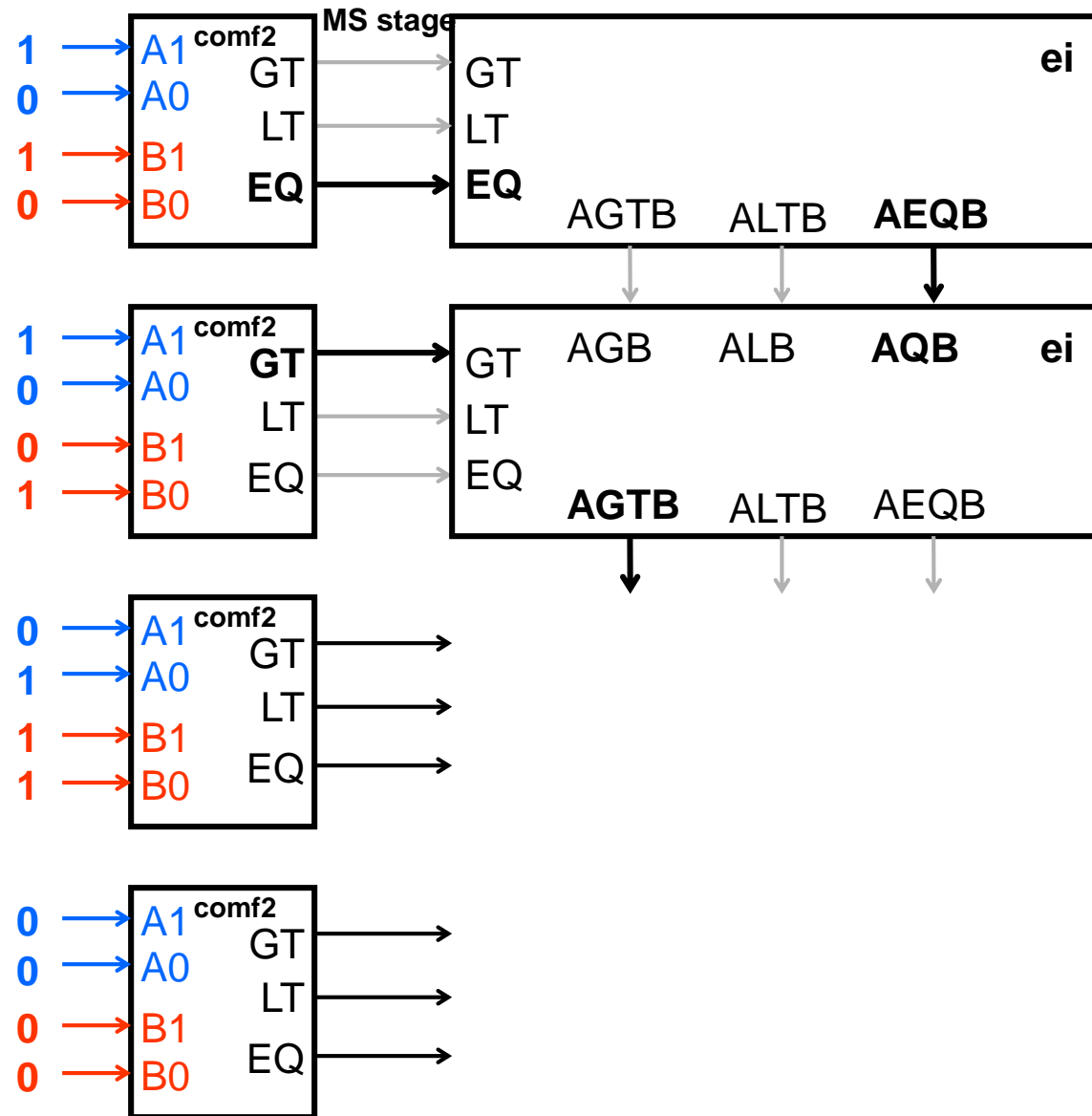


Listen to your
comparator


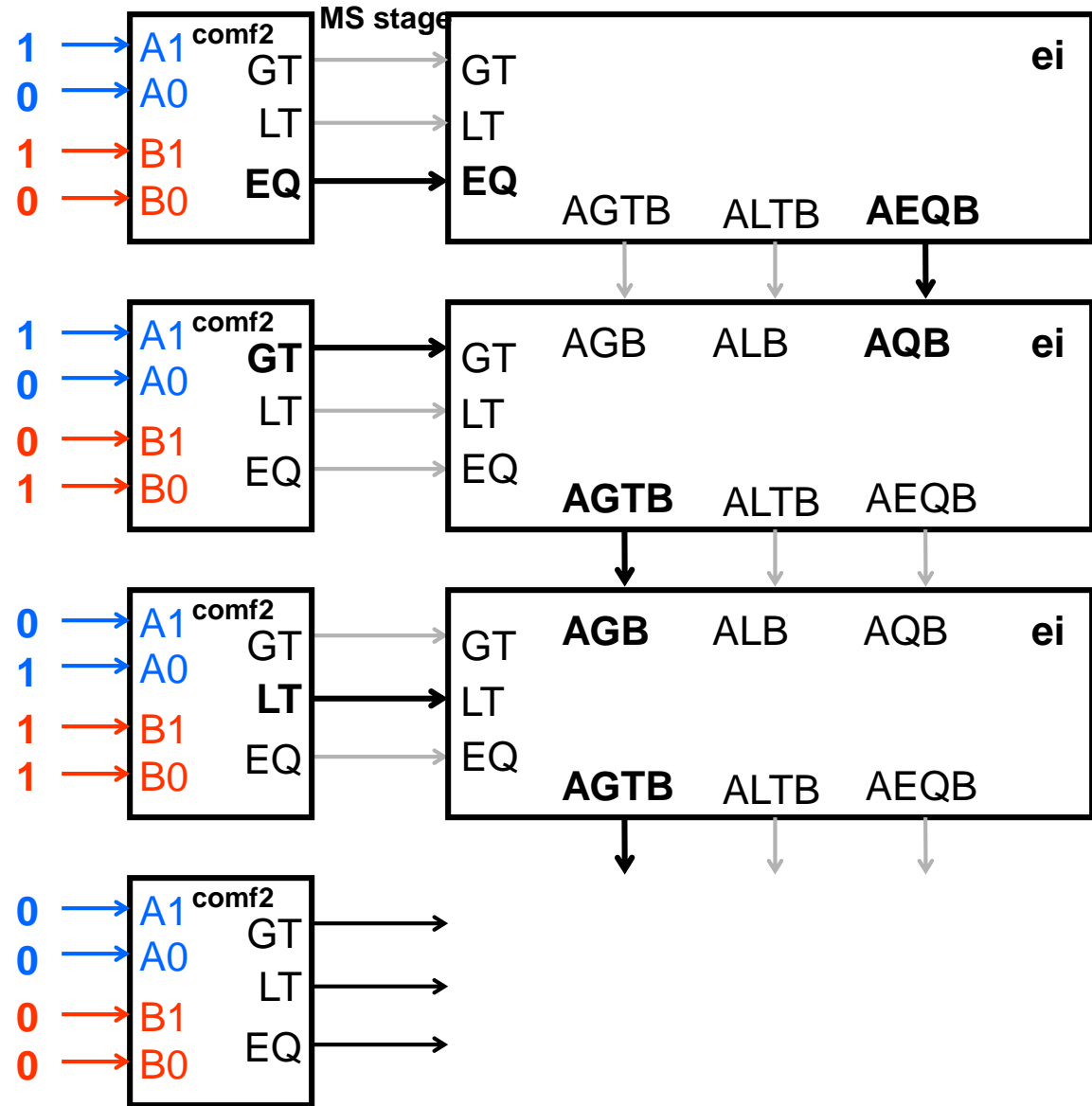


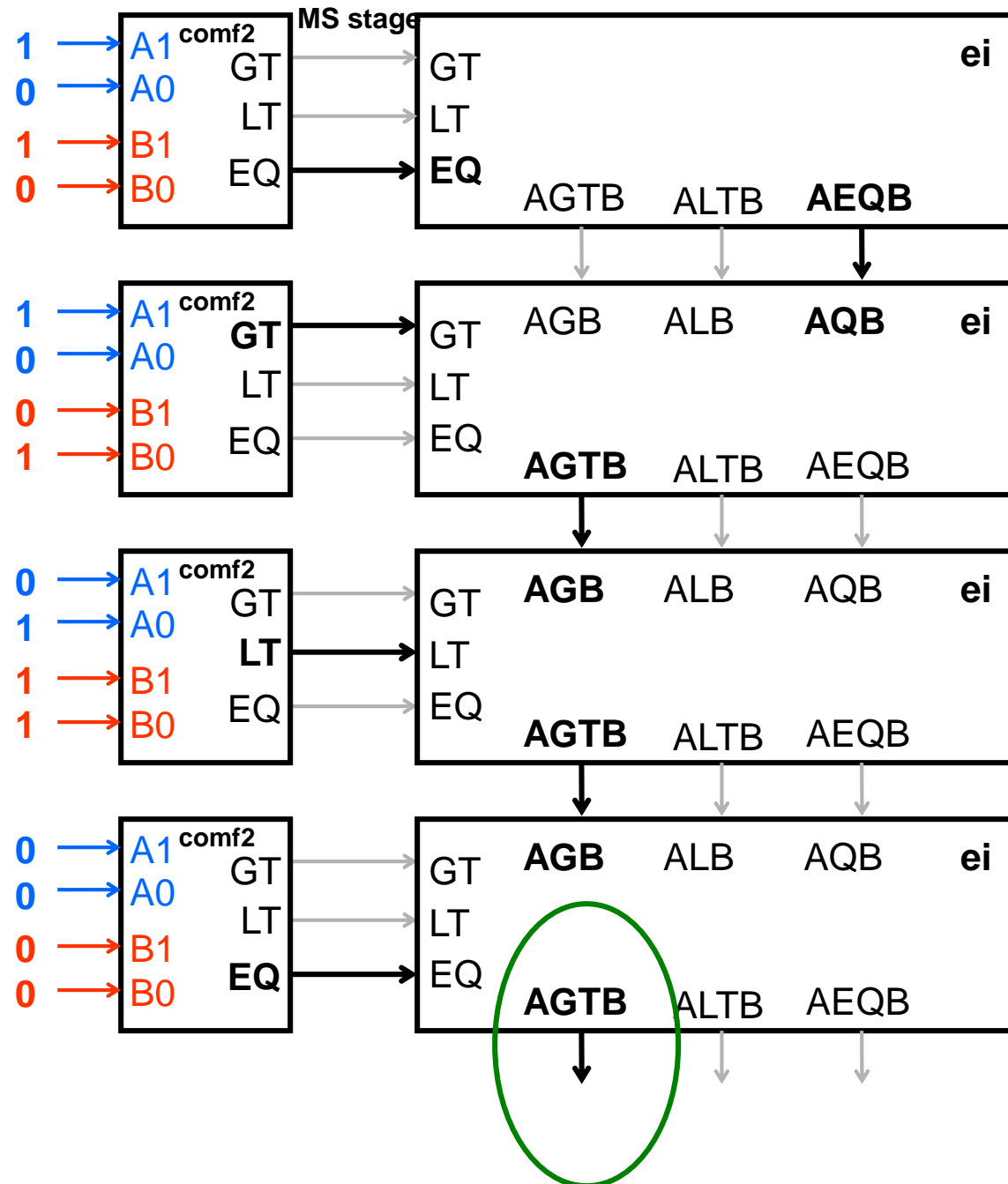

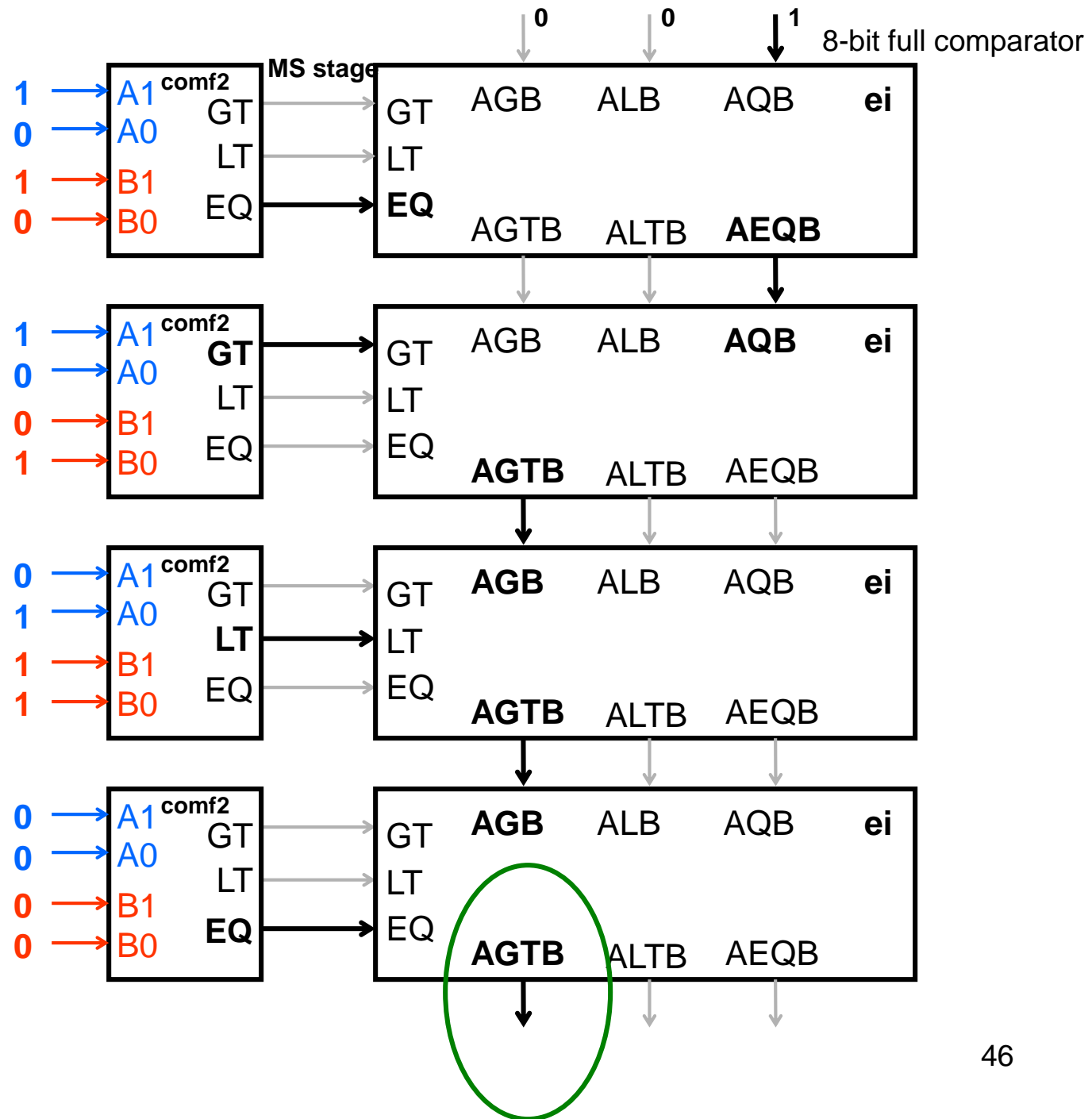


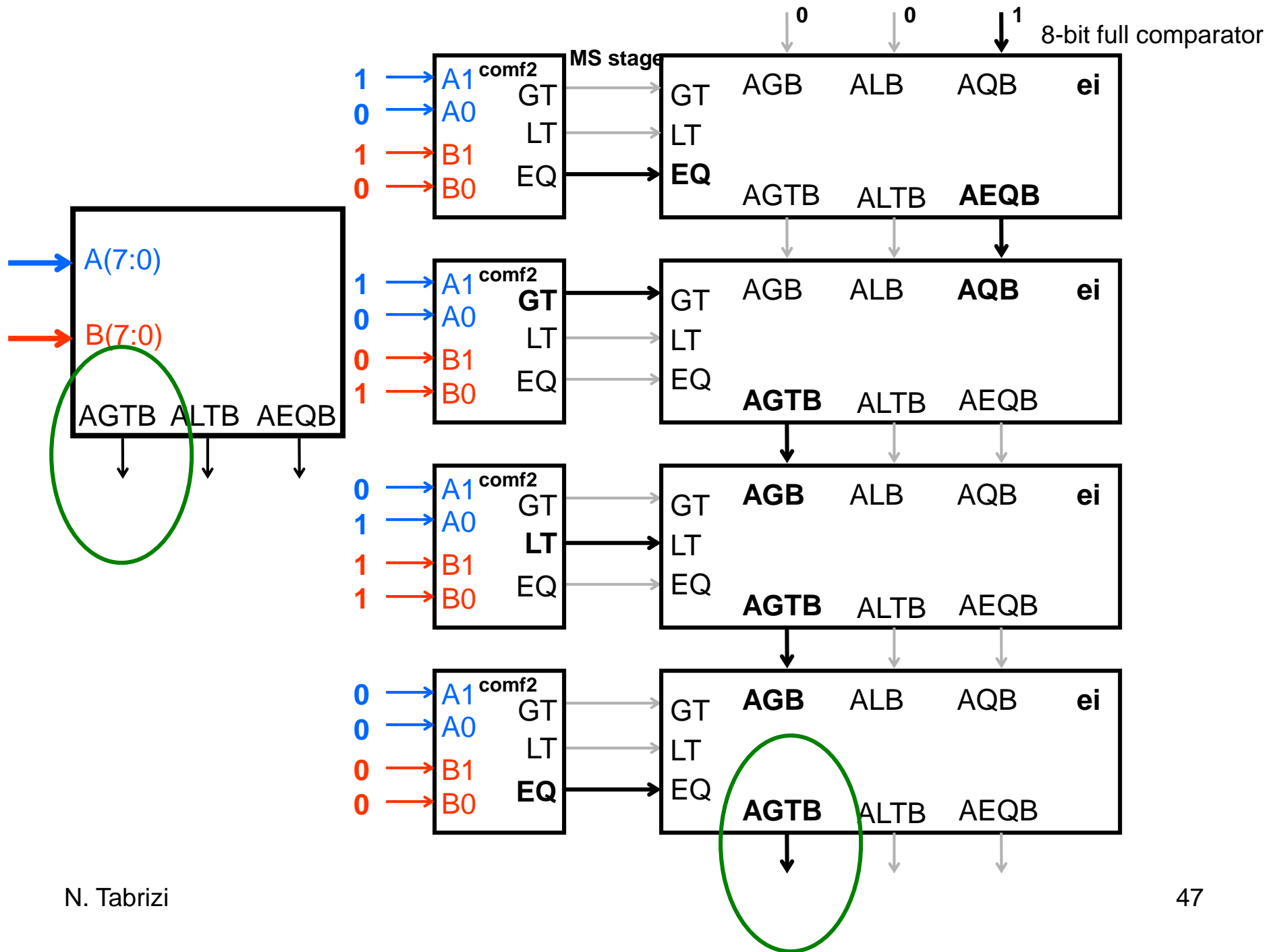

Lab-05

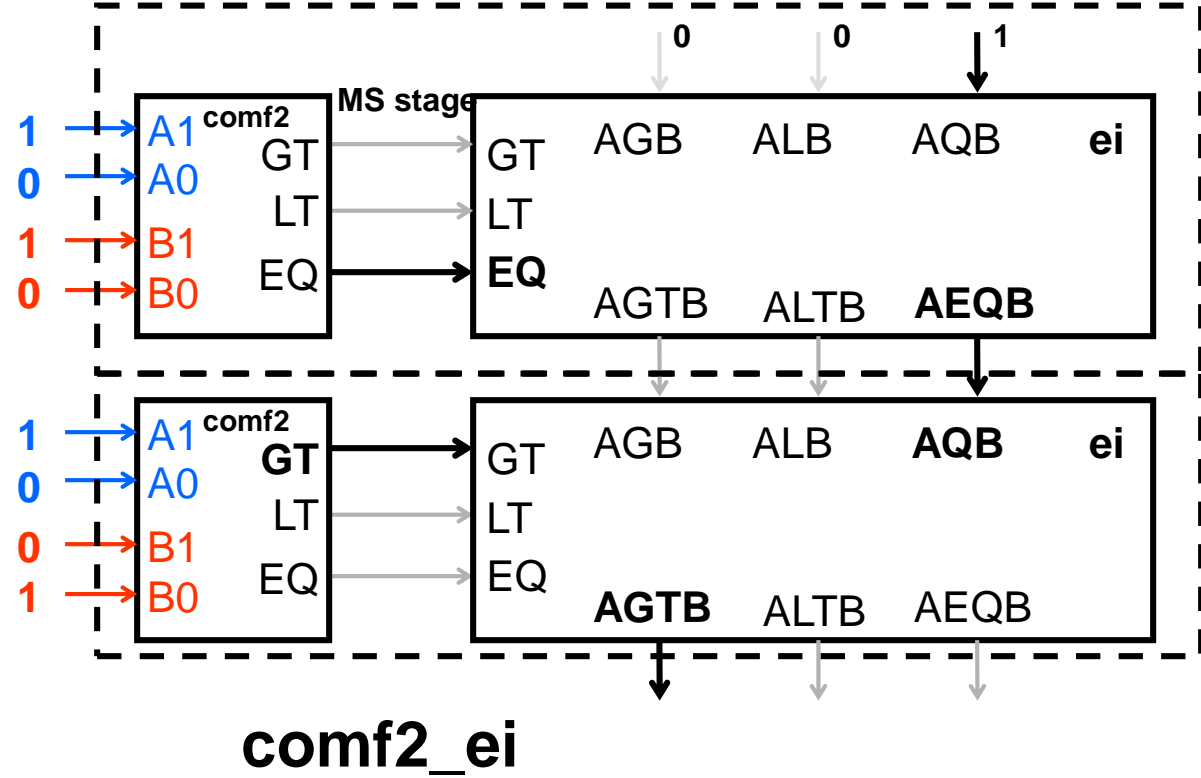 

Design of ei

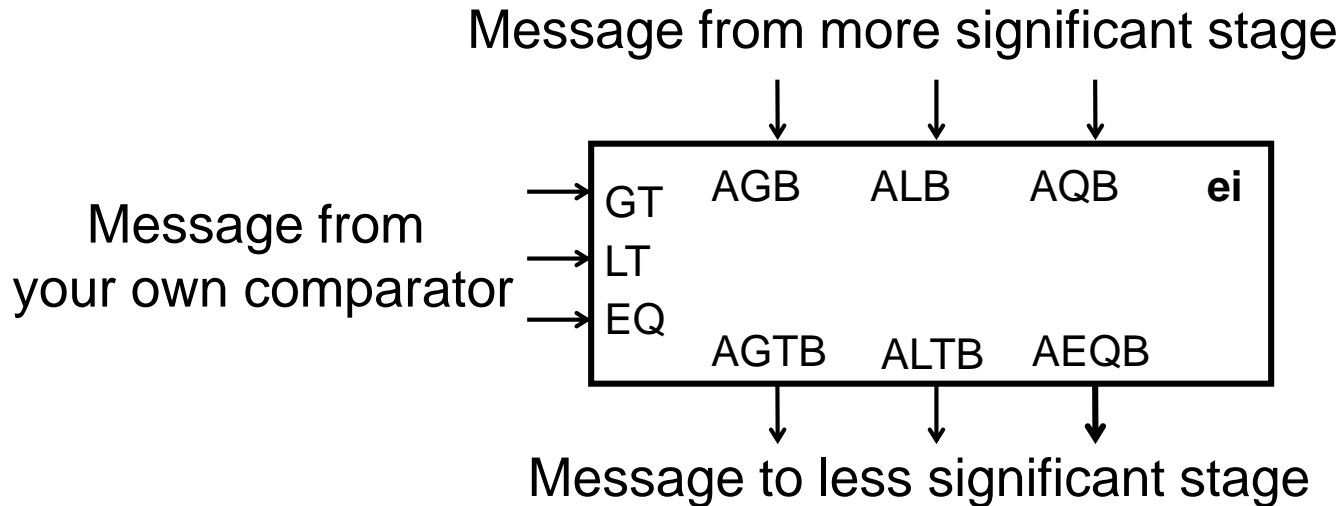

Translate the **Rule** into 3 functions:

Rule: If the more significant ei says A equals B so far, listen to your own comf2; otherwise listen to the more significant ei.

End of Chapter 4, Part II