

Digital Systems I

Lab08 Slides based on **Chapter 7 - Part II**

Behavioral Modeling

Process Constructs

IF THEN ELSE Statement

N. Tabrizi

Kettering University


IF-THEN-ELSE Statement

```
ENTITY mux4_1 IS
    PORT (A      : IN      STD_LOGIC_VECTOR (3 DOWNTO 0);
          Sel    : IN      STD_LOGIC_VECTOR (1 DOWNTO 0);
          M      : OUT     STD_LOGIC
    );
END mux4_1;
```

```
ARCHITECTURE Behavior OF mux4_1 IS
BEGIN
```

```
.
.
.
```

```
END Behavior;
```

 

IF-THEN-ELSE Statement

ARCHITECTURE Behavior OF mux4_1 IS

BEGIN

PROCESS (A, Sel)

-- *** Sensitivity list ***

BEGIN

IF Sel = "00" THEN M <= A(0);

ELSIF Sel = "01" THEN
M <= A(1);


ELSIF Sel = "10" THEN
M <= A(2);

ELSE
M <= A(3);

END IF;

END PROCESS;

END Behavior;

 

D-latch


```
ENTITY dmem IS
    PORT ( D, clk : IN    STD_LOGIC;
           Q : OUT   STD_LOGIC
         );
END dmem;
```

```
ARCHITECTURE Behavior OF dmem IS
BEGIN
```

```
    PROCESS (D, clk)
    BEGIN
```

```
        IF clk = '1' THEN
            Q <= D;
        ELSE
            Q <= Q;
        END IF;
```

```
    END PROCESS;
END Behavior;
```

 


D-latch

```
ENTITY dmem IS
    PORT ( D, clk : IN    STD_LOGIC;
           Q : OUT   STD_LOGIC
         );
END dmem;
```


```
ARCHITECTURE Behavior OF dmem IS
BEGIN
    PROCESS (D, clk)
    BEGIN
        IF clk = '1' THEN
            Q <= D;

        END IF;

    END PROCESS;
END Behavior;
```

 

Do not build FFs!

 

D-FF


```
ENTITY dmem IS
  PORT ( D, clk : IN    STD_LOGIC;
         Q : OUT   STD_LOGIC
        );
END dmem;
```

```
ARCHITECTURE Behavior OF dmem IS
BEGIN
```

```
  PROCESS (clk)
  BEGIN
```

```
    IF clk'EVENT AND clk = '1' THEN
      Q <= D;
    ELSE
      Q <= Q;
    END IF;
```

```
  END PROCESS;
END Behavior;
```

 

D-FF

```
ENTITY dmem IS
  PORT ( D, clk : IN    STD_LOGIC;
         Q : OUT   STD_LOGIC
        );
END dmem;
```


```
ARCHITECTURE Behavior OF dmem IS
BEGIN
```

```
  PROCESS (clk)
  BEGIN
```

```
    IF clk'EVENT AND clk = '1' THEN
      Q <= D;
```

```
    END IF;
```

```
  END PROCESS;
END Behavior;
```

 


D-FF with asynchronous reset

```
ARCHITECTURE Behavior OF dmem IS
BEGIN
  PROCESS (clk, R) -- R is asynchronous
  BEGIN
```

```
    IF R = '1' THEN
      Q <= '0';
    ELSIF clk'EVENT AND clk = '1' THEN
      Q <= D;
    ELSE
      Q <= Q;
    END IF;
```

```
  END PROCESS;
END Behavior;
```

 


D-FF with asynchronous reset

```
ARCHITECTURE Behavior OF dmem IS
BEGIN
  PROCESS (clk, R) -- R is asynchronous
  BEGIN
```

```
    IF R = '1' THEN
      Q <= '0';
    ELSIF clk'EVENT AND clk = '1' THEN
      Q <= D;
    END IF;
```

```
  END PROCESS;
END Behavior;
```

 


D-FF with asynchronous and synchronous resets

```
ARCHITECTURE Behavior OF dmem IS
BEGIN
  PROCESS (clk, R) -- R is asynchronous
  BEGIN
```

```
    IF R = '1' THEN
      Q <= '0';
    ELSIF clk'EVENT AND clk = '1' THEN
      IF C_n = '0' THEN
        Q <= '0';
      ELSE
        Q <= D;
      END IF;
    ELSE
      Q <= Q;
    END IF;
```

```
  END PROCESS;
END Behavior;
```

 


D-FF with asynchronous and synchronous resets

```
ARCHITECTURE Behavior OF dmem IS
BEGIN
  PROCESS (clk, R) -- R is asynchronous
  BEGIN
```

```
    IF R = '1' THEN
      Q <= '0';
    ELSIF clk'EVENT AND clk = '1' THEN
      IF C_n = '0' THEN
        Q <= '0';
      ELSE
        Q <= D;
      END IF;
    END IF;
```

```
  END PROCESS;
END Behavior;
```

 

End of Chapter 7, Part II